

# The Natural and Step Response of RL and RC Circuits

## Drill Exercises

DE 5.1 [a]  $i_g = 8e^{-300t} - 8e^{-1200t}$  A

$$v = L \frac{di_g}{dt} = -9.6e^{-300t} + 38.4e^{-1200t} \text{ V}, \quad t > 0^+$$

$$v(0^+) = -9.6 + 38.4 = 28.8 \text{ V}$$

[b]  $v = 0$  when  $38.4e^{-1200t} = 9.6e^{-300t}$  or  $t = (\ln 4)/900 = 1.54 \text{ ms}$

[c]  $p = vi = 384e^{-1500t} - 76.8e^{-600t} - 307.2e^{-2400t} \text{ W}$

[d]  $\frac{dp}{dt} = 0$  when  $e^{1800t} - 12.5e^{900t} + 16 = 0$

Let  $x = e^{900t}$  and solve the quadratic  $x^2 - 12.5x + 16 = 0$

$$x = 1.45, \quad x = 11.05, \quad t = \frac{\ln 1.45}{900} = 411.05 \mu\text{s}, \quad t = \frac{\ln 11.05}{900} = 2.67 \text{ ms}$$

$p$  is maximum at  $t = 411.05 \mu\text{s}$

[e]  $p_{\max} = 384e^{-1.5(0.41105)} - 76.8e^{-0.6(0.41105)} - 307.2e^{-2.4(0.41105)} = 32.72 \text{ W}$

[f]  $i_{\max} = 8[e^{-0.3(1.54)} - e^{-1.2(1.54)}] = 3.78 \text{ A}$

$$w_{\max} = (1/2)(4 \times 10^{-3})(3.78)^2 = 28.6 \text{ mJ}$$

[g]  $W$  is max when  $i$  is max,  $i$  is max when  $di/dt$  is zero.

When  $di/dt = 0$ ,  $v = 0$ , therefore  $t = 1.54 \text{ ms}$ .

DE 5.2 [a]  $i = C \frac{dv}{dt} = 24 \times 10^{-6} \frac{d}{dt}[e^{-15,000t} \sin 30,000t]$

$$= [0.72 \cos 30,000t - 0.36 \sin 30,000t]e^{-15,000t} \text{ A}, \quad i(0^+) = 0.72 \text{ A}$$

$$[\mathbf{b}] \quad i\left(\frac{\pi}{80} \text{ ms}\right) = -31.66 \text{ mA}, \quad v\left(\frac{\pi}{80} \text{ ms}\right) = 20.505 \text{ V},$$

$$p = vi = -649.23 \text{ mW}$$

$$[\mathbf{c}] \quad w = \left(\frac{1}{2}\right) C v^2 = 126.13 \mu\text{J}$$

---


$$\text{DE 5.3} \quad [\mathbf{a}] \quad v = \left(\frac{1}{C}\right) \int_{0^-}^t i \, dx + v(0^-)$$

$$= \frac{1}{0.6 \times 10^{-6}} \int_{0^-}^t 3 \cos 50,000x \, dx = 100 \sin 50,000t \text{ V}$$

$$[\mathbf{b}] \quad p(t) = vi = [300 \cos 50,000t] \sin 50,000t$$

$$= 150 \sin 100,000t \text{ W}, \quad p_{(\max)} = 150 \text{ W}$$

$$[\mathbf{c}] \quad w_{(\max)} = \left(\frac{1}{2}\right) C v_{\max}^2 = 0.30(100)^2 = 3000 \mu\text{J} = 3 \text{ mJ}$$

---


$$\text{DE 5.4} \quad [\mathbf{a}] \quad L_{\text{eq}} = \frac{60(240)}{300} = 48 \text{ mH}$$

$$[\mathbf{b}] \quad i(0^+) = 3 + -5 = -2 \text{ A}$$

$$[\mathbf{c}] \quad i = \frac{125}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 2 = 0.125e^{-5t} - 2.125 \text{ A}$$

$$[\mathbf{d}] \quad i_1 = \frac{50}{3} \int_{0^+}^t (-0.03e^{-5x}) \, dx + 3 = 0.1e^{-5t} + 2.9 \text{ A}$$

$$i_2 = \frac{25}{6} \int_{0^+}^t (-0.03e^{-5x}) \, dx - 5 = 0.025e^{-5t} - 5.025 \text{ A}$$

$$i_1 + i_2 = i$$

---


$$\text{DE 5.5} \quad v_1 = 0.5 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 10 = -12e^{-10t} + 2 \text{ V}$$

$$v_2 = 0.125 \times 10^6 \int_{0^+}^t 240 \times 10^{-6} e^{-10x} \, dx - 5 = -3e^{-10t} - 2 \text{ V}$$

$$v_1(\infty) = 2 \text{ V}, \quad v_2(\infty) = -2 \text{ V}$$

$$W = \left[ \frac{1}{2}(2)(4) + \frac{1}{2}(8)(4) \right] \times 10^{-6} = 20 \mu\text{J}$$

---


$$\text{DE 5.6} \quad [\mathbf{a}] \quad i = \left(\frac{120}{3+5}\right) \left(\frac{-30}{36}\right) = -12.5 \text{ A}$$

$$[\mathbf{b}] \quad w = 0.5(8 \times 10^{-3})(12.5)^2 = 625 \text{ mJ}$$

$$[\mathbf{c}] \quad \tau = \frac{L}{R} = \frac{8 \times 10^{-3}}{2} = 4 \text{ ms}$$

$$[\mathbf{d}] \quad i = -12.5e^{-250t} \text{ A}, \quad t \geq 0$$

$$[\mathbf{e}] \quad i(5 \text{ ms}) = -3.58 \text{ A}, \quad w(5 \text{ ms}) = (0.5)(8) \times 10^{-3}(3.58)^2 = 51.3 \text{ mJ}$$

$$w(\text{dis}) = 625 - 51.3 = 573.7 \text{ mJ}$$

$$\% \text{ dissipated} = \left( \frac{573.7}{625} \right) 100 = 91.8\%$$

DE 5.7    $[\mathbf{a}] \quad i_L(0^-) = 6.4 \left( \frac{10}{16} \right) = 4 \text{ A} = i_L(0^+), \quad t > 0$

$$R_{\text{eq}} = \frac{(4)(16)}{20} = 3.2 \Omega, \quad \tau = \frac{0.32}{3.2} = 0.1 \text{ s}$$

$$\text{Therefore } \frac{1}{\tau} = 10, \quad i_L = 4e^{-10t} \text{ A}$$

Let  $i_1$  equal the current in the  $10 \Omega$  resistor. Let the reference direction for  $i_1$  be up. Then

$$i_1 = \left( \frac{4}{20} \right) i_L = 0.8e^{-10t} \text{ A}, \quad v_o = -10i_1 = -8e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad v_{4\Omega} = L \frac{di_L}{dt} = 0.32(-40)e^{-10t} = -12.8e^{-10t} \text{ V}, \quad t \geq 0^+$$

$$p_{4\Omega} = \frac{v_{4\Omega}^2}{4} = 40.96e^{-20t} \text{ W}, \quad t \geq 0^+$$

$$w_{4\Omega} = \int_0^\infty 40.96e^{-20t} dt = 2.048 \text{ J}$$

$$w_i = \frac{1}{2} Li^2 = \frac{1}{2}(0.32)(16) = 2.56 \text{ J}$$

$$\% \text{ dissipated} = \left( \frac{2.048}{2.56} \right) 100 = 80\%$$

DE 5.8    $[\mathbf{a}] \quad v(0) = \left[ \frac{7.5(80)}{150} \right] 50 = 200 \text{ V}$

$$[\mathbf{b}] \quad \tau = RC = (50 \times 10^3)(0.4 \times 10^{-6}) = 20 \text{ ms}$$


$$[\mathbf{c}] \quad v = 200e^{-50t} \text{ V}$$

$$[\mathbf{d}] \quad w(0) = 0.5(0.4 \times 10^{-6})(200)^2 = 8 \text{ mJ}$$

$$[\mathbf{e}] \quad w(t) = 0.5(0.4 \times 10^{-6})(4 \times 10^4)e^{-100t} = 8e^{-100t} \text{ mJ}$$

$$8e^{-100t} = 2, \quad t = (\ln 4)/100 = 13.86 \text{ ms}$$

DE 5.9 [a] For  $t < 0$ :

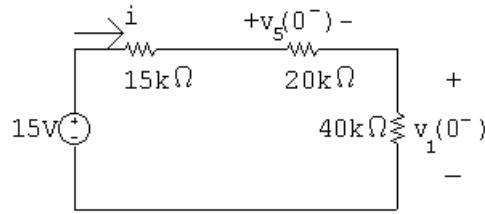

$$i = \frac{15}{75,000} = \frac{1}{5} \text{ mA}, \quad v_5(0^-) = 4 \text{ V}, \quad v_1(0^-) = 8 \text{ V}$$

$$\tau_5 = (20 \times 10^3)(5 \times 10^{-6}) = 100 \text{ ms}, \quad 1/\tau_5 = 10$$

$$\tau_1 = (40 \times 10^3)(1 \times 10^{-6}) = 40 \text{ ms}, \quad 1/\tau_1 = 25$$

$$\text{Therefore } v_5 = 4e^{-10t} \text{ V}, \quad t \geq 0; \quad v_1 = 8e^{-25t} \text{ V}, \quad t \geq 0;$$

$$v_o = v_1 + v_5 = [8e^{-25t} + 4e^{-10t}] \text{ V}, \quad t \geq 0$$

[b]  $v_1(60 \text{ ms}) \cong 1.79 \text{ V}, \quad v_5(60 \text{ ms}) \cong 2.20 \text{ V}$

$$w_1(60 \text{ ms}) = (1/2)(1)(1.79)^2 \cong 1.59 \mu\text{J}$$

$$w_5(60 \text{ ms}) = (1/2)(5)(2.20)^2 \cong 12.05 \mu\text{J}$$

$$w_1(0) = \frac{1}{2}(10^{-6})(64) + \frac{1}{2}(5 \times 10^{-6})(16) = 72 \mu\text{J}$$

$$w_{\text{diss}} = 72 - 13.64 = 58.36 \mu\text{J}$$

$$\% \text{ dissipated} = (58.36/72)(100) = 81.05 \%$$

DE 5.10 [a]  $i(0^+) = 24/2 = 12 \text{ A}$


[b]  $v(0^+) = -10(8 + 12) = -200 \text{ V}$

[c]  $\tau = L/R = (200/10) \times 10^{-3} = 20 \text{ ms}$

[d]  $i = -8 + [12 - (-8)]e^{-50t} = [-8 + 20e^{-50t}] \text{ A}, \quad t \geq 0^+$

[e]  $v = 0 + [-200 - 0]e^{-50t} \text{ V} = -200e^{-50t} \text{ V}, \quad t \geq 0^+$

DE 5.11 [a]

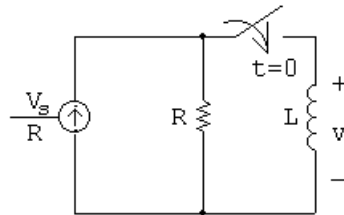

$$\frac{v}{R} + \frac{1}{L} \int_0^t v \, dx = \frac{V_s}{R}$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} = 0$$

$$\frac{dv}{dt} + \frac{R}{L}v = 0$$

$$[\mathbf{b}] \quad \frac{dv}{dt} = -\frac{R}{L}v$$

$$\frac{dv}{dt} dt = -\frac{R}{L}v dt$$

$$\therefore \quad \frac{dv}{v} = -\frac{R}{L} dt$$

$$\int_{v(0^+)}^{v(t)} \frac{dy}{y} = -\frac{R}{L} \int_{0^+}^t dx$$


$$\ln y \Big|_{v(0^+)}^{v(t)} = -\left(\frac{R}{L}\right)t$$

$$\ln \left[ \frac{v(t)}{v(0^+)} \right] = -\left(\frac{R}{L}\right)t$$

$$v(t) = v(0^+)e^{-(R/L)t}; \quad v(0^+) = \left(\frac{V_s}{R} - I_o\right)R = V_s - I_oR$$

$$\therefore \quad v(t) = (V_s - I_oR)e^{-(R/L)t}$$

DE 5.12 [a]

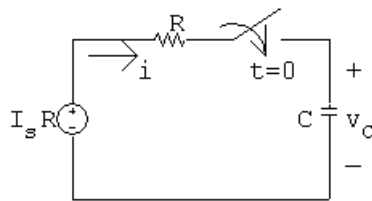

$$I_s R = Ri + \frac{1}{C} \int_{0^+}^t i dx + V_o$$

$$0 = R \frac{di}{dt} + \frac{i}{C} + 0$$

$$\therefore \quad \frac{di}{dt} + \frac{i}{RC} = 0$$

$$[\mathbf{b}] \quad \frac{di}{dt} = -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC}$$


$$\int_{i(0^+)}^{i(t)} \frac{dy}{y} = -\frac{1}{RC} \int_{0^+}^t dx$$

$$\ln \frac{i(t)}{i(0^+)} = \frac{-t}{RC}$$

$$i(t) = i(0^+)e^{-t/RC}; \quad i(0^+) = \frac{I_s R - V_o}{R} = \left(I_s - \frac{V_o}{R}\right)$$

$$\therefore i(t) = \left(I_s - \frac{V_o}{R}\right) e^{-t/RC}$$

DE 5.13 [a]

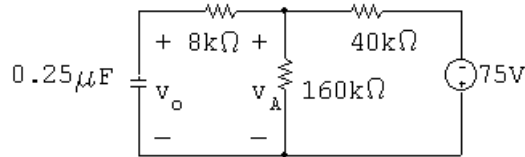

$$v_o = -60 + 90e^{-100t} \text{ V}$$

$$\frac{v_A - v_o}{8000} + \frac{v_A}{160,000} + \frac{v_A + 75}{40,000} = 0$$

$$20v_A - 20v_o + v_A + 4v_A + 300 = 0$$

$$25v_A = 20v_o - 300$$

$$v_A = 0.8v_o - 12$$

$$v_A = -48 + 72e^{-100t} - 12 = -60 + 72e^{-100t} \text{ V}, \quad t \geq 0^+$$

[b]  $t \geq 0^+$

DE 5.14 [a]  $v_c(0^+) = 50 \text{ V}$

[b]  $v_c(\infty) = \left(-\frac{30}{25}\right) 20 = -24 \text{ V}$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$v_{\text{Th}} = -24 \text{ V}, \quad R_{\text{Th}} = 20 \parallel 5 = 4 \Omega,$$

$$\text{Therefore } \tau = 4(25 \times 10^{-9}) = 0.1 \mu\text{s}$$

[d]  $i(0^+) = -\frac{50 + 24}{4} = -18.5 \text{ A}$

[e]  $v_c = -24 + [50 - (-24)]e^{-t/\tau} = -24 + 74e^{-10^7 t} \text{ V}, \quad t \geq 0$

[f]  $i = -18.5e^{-t/\tau} = -18.5e^{-10^7 t} \text{ A}, \quad t \geq 0^+$

DE 5.15 [a]  $v_c(0^+) = (9/12)(120) = 90 \text{ V}$

[b]  $v_c(\infty) = -1.5(40) = -60 \text{ V}$

- [c] Find the Thévenin equivalent with respect to the terminals of the capacitor:


$$v_{\text{Th}} = -60 \text{ V}, \quad R_{\text{Th}} = 50 \text{ k}\Omega$$

$$\tau = R_{\text{Th}}C = 1 \text{ ms} = 1000 \mu\text{s}$$

[d]  $v_c = -60 + (90 + 60)e^{-1000t} = -60 + 150e^{-1000t} \text{ V}, \quad t \geq 0$

Therefore  $t = \frac{\ln(150/60)}{1000} = 916.3 \mu\text{s}$

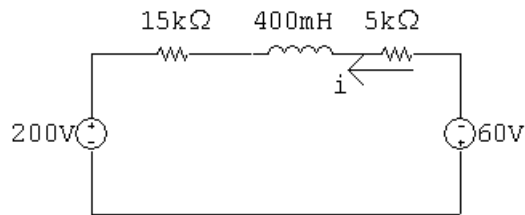
- DE 5.16 [a] For  $t < 0$ , calculate the Thévenin equivalent for the circuit to the left and right of the 400-mH inductor. We get



$$i(0^-) = -260/20 = -13 \text{ mA}$$

$$i(0^-) = i(0^+) = -13 \text{ mA}$$

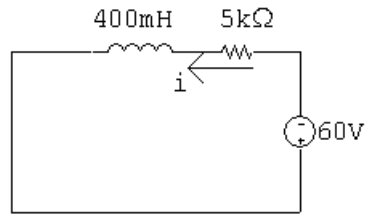- [b] For  $t > 0$ , the circuit reduces to



Therefore  $i(\infty) = -60/5 = -12 \text{ mA}$

[c]  $\tau = (400/5) \times 10^{-6} = 80 \mu\text{s}$

[d]  $i(t) = -12 + [-13 + 12]e^{-12,500t} = -12 - e^{-12,500t} \text{ mA}, \quad t \geq 0$

## Problems

P 5.1  $p = vi = 40t[e^{-10t} - 10te^{-20t} - e^{-20t}]$



$$W = \int_0^\infty p \, dx = \int_0^\infty 40x[e^{-10x} - 10xe^{-20x} - e^{-20x}] \, dx = 0.2 \text{ J}$$

This is energy stored in the inductor at  $t = \infty$ .

P 5.2  $0 \leq t < \infty$

$$i_L = \frac{10^3}{4} \int_0^t 30 \times 10^{-3} e^{-3x} \, dx + 2.5 = 7.5 \frac{e^{-3x}}{-3} \Big|_0^t + 2.5$$
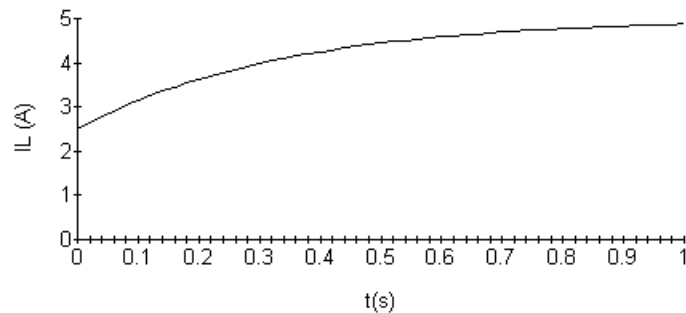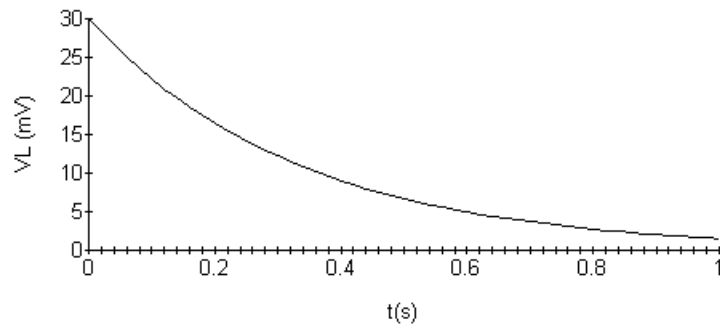
$$= 5 - 2.5e^{-3t} \text{ A}, \quad 0 \leq t \leq \infty$$



P 5.3 [a]  $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 50[t(-10e^{-10t}) + e^{-10t}] = 50e^{-10t}(1 - 10t)$$



$$\begin{aligned}
 v &= (2 \times 10^{-3})(50)e^{-10t}(1 - 10t) \\
 &= 100e^{-10t}(1 - 10t) \text{ mV}, \quad t > 0
 \end{aligned}$$

[b]  $p = vi$

$$v(200 \text{ ms}) = 100e^{-2}(1 - 2) = -13.53 \text{ mV}$$

$$i(200 \text{ ms}) = 50(0.2)e^{-2} = 1.35 \text{ A}$$

$$p(200 \text{ ms}) = -13.53 \times 10^{-3}(1.35) = -18.32 \text{ mW}$$

[c] delivering

[d]  $w = \frac{1}{2}Li^2 = \frac{1}{2}(2 \times 10^{-3})(1.35)^2 = 1.83 \text{ mJ}$

[e]  $\frac{di}{dt} = 0$  when  $t = \frac{1}{10} \text{ s} = 100 \text{ ms}$

$$i_{\max} = 50(0.1)e^{-1} = 1.84 \text{ A}$$

$$w_{\max} = \frac{1}{2}(2 \times 10^{-3})(1.84)^2 = 3.38 \text{ mJ}$$

P 5.4 [a]  $0 \leq t \leq 1 \text{ ms} :$

$$\begin{aligned}
 i &= \frac{1}{L} \int_0^t v_s dx + i(0) = \frac{10^6}{300} \int_0^t 6 \times 10^{-3} dx + 0 \\
 &= 20x \Big|_0^t = 20t \text{ A}
 \end{aligned}$$

$1 \text{ ms} \leq t \leq 2 \text{ ms} :$


$$i = \frac{10^6}{300} \int_{10^{-3}}^t (12 \times 10^{-3} - 6x) dx + 20 \times 10^{-3}$$

$$\therefore i = 40t - 10,000t^2 - 10 \times 10^{-3} \text{ A}$$

$2 \text{ ms} \leq t \leq \infty :$

$$i = \frac{10^6}{300} \int_{2 \times 10^{-3}}^t (0) dx + 30 \times 10^{-3} = 30 \text{ mA}$$

[b]

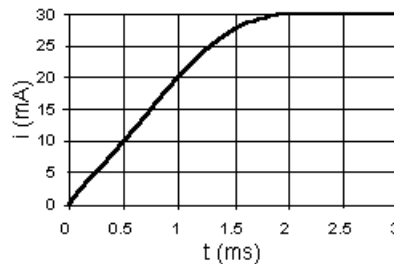

P 5.5 [a]  $i = 0 \quad t < 0$   
 $i = 16t \text{ A} \quad 0 \leq t \leq 25 \text{ ms}$   
 $i = 0.8 - 16t \text{ A} \quad 25 \leq t \leq 50 \text{ ms}$   
 $i = 0 \quad 50 \text{ ms} < t$

[b]  $v = L \frac{di}{dt} = 375 \times 10^{-3}(16) = 6 \text{ V} \quad 0 \leq t \leq 25 \text{ ms}$

$$v = 375 \times 10^{-3}(-16) = -6 \text{ V} \quad 25 \leq t \leq 50 \text{ ms}$$

$$v = 0 \quad t < 0$$

$$v = 6 \text{ V} \quad 0 < t < 25 \text{ ms}$$

$$v = -6 \text{ V} \quad 25 < t < 50 \text{ ms}$$

$$v = 0 \quad 50 \text{ ms} < t$$

$$p = vi$$

$$p = 0 \quad t < 0$$

$$p = (16t)(6) = 96t \text{ W} \quad 0 < t < 25 \text{ ms}$$

$$p = (0.8 - 16t)(-6) = 96t - 4.8 \text{ W} \quad 25 < t < 50 \text{ ms}$$

$$p = 0 \quad 50 \text{ ms} < t$$

$$w = 0 \quad t < 0$$

$$w = \int_0^t (16x)6 \, dx = 96 \frac{x^2}{2} \Big|_0^t = 48t^2 \text{ J} \quad 0 < t < 25 \text{ ms}$$

$$w = \int_{0.025}^t (96x - 4.8) \, dx + 0.03$$

$$= \int_{0.025}^t 96x \, dx - \int_{0.025}^t 4.8 \, dx + 0.03$$

$$= 96 \frac{x^2}{2} \Big|_{0.025}^t - 4.8x \Big|_{0.025}^t + 0.03$$

$$= 48t^2 - 4.8t + 0.12 \text{ J} \quad 25 < t < 50 \text{ ms}$$

$$w = 0 \quad 50 \text{ ms} < t$$

P 5.6 [a]  $0 \leq t \leq 1 \text{ s} :$

$$v = -100t$$

$$i = \frac{1}{5} \int_0^t -100x \, dx + 0 = -20 \frac{x^2}{2} \Big|_0^t$$

$$i = -10t^2 \text{ A}$$

$$1 \text{ s} \leq t \leq 3 \text{ s} :$$

$$v = -200 + 100t$$

$$i(1) = -10 \text{ A}$$

$$\begin{aligned} \therefore i &= \frac{1}{5} \int_1^t (100x - 200) dx - 10 \\ &= 20 \int_1^t x dx - 40 \int_1^t dx - 10 \\ &= 10(t^2 - 1) - 40(t - 1) - 10 \\ &= 10t^2 - 40t + 20 \text{ A} \end{aligned}$$

$$3 \text{ s} \leq t \leq 5 \text{ s} :$$

$$v = 100$$

$$i(3) = 10(9) - 120 + 20 = -10 \text{ A}$$

$$\begin{aligned} i &= \frac{1}{5} \int_3^t 100 dx - 10 \\ &= 20t - 60 - 10 = 20t - 70 \text{ A} \end{aligned}$$

$$5 \text{ s} \leq t \leq 6 \text{ s} :$$


$$v = -100t + 600$$

$$i(5) = 100 - 70 = 30$$

$$\begin{aligned} i &= \frac{1}{5} \int_5^t (-100x + 600) dx + 30 \\ &= -20 \int_5^t x dx + 120 \int_5^t dx + 30 \\ &= -10(t^2 - 25) + 120(t - 5) + 30 \\ &= -10t^2 + 120t - 320 \text{ A} \end{aligned}$$

$$[\mathbf{b}] \quad i(6) = -10(36) + 120(6) - 320 = 720 - 680 = 40 \text{ A}, \quad 6 \leq t \leq \infty$$

[c]

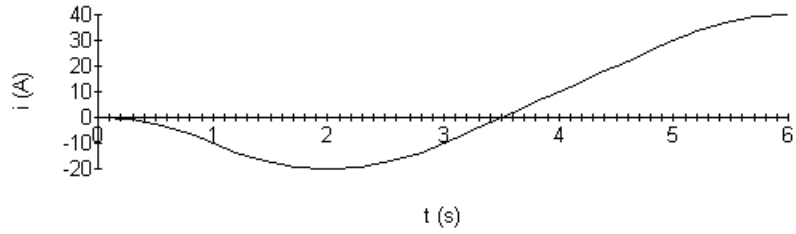

P 5.7 [a]  $i(0) = A_1 + A_2 = 0.05$

$$\frac{di}{dt} = -2500A_1e^{-2500t} - 7500A_2e^{-7500t}$$

$$v = -50A_1e^{-2500t} - 150A_2e^{-7500t} \text{ V}$$

$$v(0) = -50A_1 - 150A_2 = 10$$

$$\therefore -5A_1 - 15A_2 = 1$$

But from the equation for  $i(0)$ ,  $5A_1 + 5A_2 = 0.25$

Solving,  $A_1 = 0.175$  and  $A_2 = -0.125$

Thus,

$$i = 0.175e^{-2500t} - 0.125e^{-7500t} \text{ A}, \quad t \geq 0$$

$$v = -8.75e^{-2500t} + 18.75e^{-7500t} \text{ V}, \quad t \geq 0$$

[b]  $p = vi = 4.375e^{-10,000t} - 1.53125e^{-5000t} - 2.34375e^{-15,000t} \text{ W}$

$$p = 0 \quad \text{when} \quad 4.375e^{-10,000t} - 1.53125e^{-5000t} - 2.34375e^{-15,000t} = 0$$

Let  $x = e^{5000t}$ , then

$$4.375x - 1.53125x^2 - 2.34375 = 0$$

Solving,

$$x = 0.7143, \quad x = 2.143$$

If  $x < 1$ ,  $t$  must be negative hence the solution for  $t > 0$  must be  $x = 2.143$

$$e^{5000t} = 2.143 \quad \text{so} \quad t = 152.43 \mu\text{s}$$

P 5.8 [a] From Prob. 5.7 we have

$$i = A_1 e^{-2500t} + A_2 e^{-7500t} \text{ A}$$

$$v = -50A_1 e^{-2500t} - 150A_2 e^{-7500t} \text{ V}$$

$$i(0) = A_1 + A_2 = 0.05$$

$$v(0) = -50A_1 - 150A_2 = -100$$

$$\therefore A_1 + A_2 = 0.05 \quad \text{and} \quad A_1 + 3A_2 = 2$$

$$\therefore A_2 = 0.975 \text{ A}, \quad A_1 = -0.925 \text{ A}$$

Thus,

$$i = -0.925e^{-2500t} + 0.975e^{-7500t} \text{ A} \quad t \geq 0$$



$$v = 46.25e^{-2500t} - 146.25e^{-7500t} \text{ V} \quad t \geq 0$$

[b]  $i = 0$  when  $0.975e^{-7500t} = 0.925e^{-2500t}$

$$\therefore e^{5000t} = 1.0541$$

$$t = (\ln 1.054)/5000 = 10.53 \mu\text{s}$$

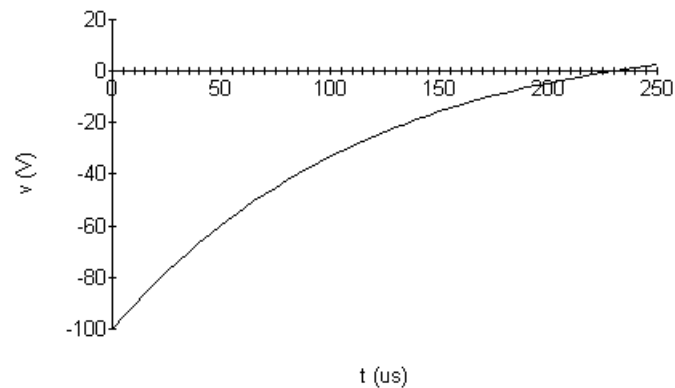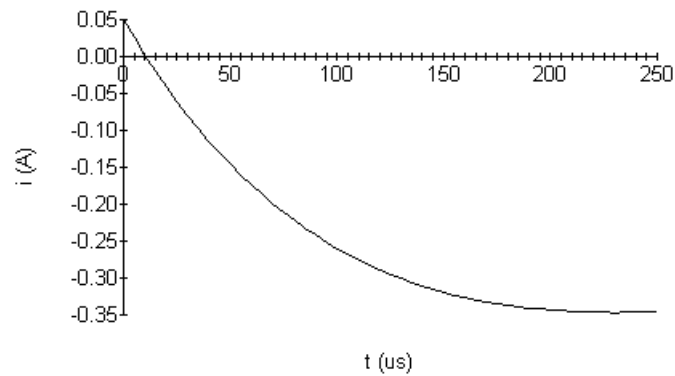$v = 0$  when  $46.25e^{-2500t} = 146.25e^{-7500t}$



$\therefore$  Energy is being stored between  $10.53 \mu\text{s}$  and  $230.25 \mu\text{s}$ ; energy is being extracted between 0 and  $10.53 \mu\text{s}$  and between  $230.25 \mu\text{s}$  and infinity.

$$[\text{c}] \quad p = vi = 180.375e^{-10,000t} - 42.78125e^{-5000t} - 142.59375e^{-15,000t} \text{ W}$$

$$\therefore W_{\text{stored}} = \int_{t_1}^{t_2} p dt + w(0)$$

$$\begin{aligned} W_{\text{stored}} &= 10^{-3} \left\{ -18.0375e^{-10,000t} \Big|_{t_1}^{t_2} + 8.55625e^{-5000t} \Big|_{t_1}^{t_2} + \right. \\ &\quad \left. 9.50625e^{-15,000t} \Big|_{t_1}^{t_2} \right\} + 25 \times 10^{-6} \\ &= 8.55625e^{-5000t_2} + 9.50625e^{-15,000t_2} - 18.0375e^{-10,000t_2} \\ &\quad - 8.55625e^{-5000t_1} - 9.50625e^{-15,000t_1} + 18.0375e^{-10,000t_1} \\ &\quad + 0.025 \text{ mW} \end{aligned}$$

$$\text{where } t_1 = 10.52 \mu\text{s}, \quad t_2 = 230.11 \mu\text{s}$$

$$W_{\text{stored}} = 1.23 \text{ mJ.}$$

$$\begin{aligned} W_{\text{extracted}} &= \int_0^{t_1} p dt + \int_{t_2}^{\infty} p dt \\ &= \int_0^{t_1} (180.375e^{-10^4 t} - 42.78125e^{-5000t} \\ &\quad - 142.59375e^{-15,000t}) dt \\ &\quad + \int_{t_2}^{\infty} (180.375e^{-10^4 t} - 42.78125e^{-5000t} \\ &\quad - 142.59375e^{-15,000t}) dt \\ &= 10^{-3} \left\{ -18.0375e^{-10,000t} \Big|_0^{t_1} + 8.55625e^{-5000t} \Big|_0^{t_1} \right. \\ &\quad + 9.50625e^{-15,000t} \Big|_0^{t_1} - 18.0375e^{-10,000t} \Big|_{t_2}^{\infty} \\ &\quad + 8.55625e^{-5000t} \Big|_{t_2}^{\infty} + 9.50625e^{-15,000t} \Big|_{t_2}^{\infty} \left. \right\} \\ &= \{ 18.0375e^{-10,000t_2} - 8.55625e^{-5000t_2} - 9.50625e^{-15,000t_2} \\ &\quad + 8.55625e^{-5000t_1} + 9.50625e^{-15,000t_1} - 18.0375e^{-10,000t_1} \\ &\quad - 0.025 \} \text{ mJ} \end{aligned}$$

$$W_{\text{ext.}} = -1.23 \text{ mJ} \quad \therefore W_{\text{stored}} = W_{\text{extracted}}$$

P 5.9 [a]  $v_L = L \frac{di}{dt} = [125 \sin 400t]e^{-200t} \text{ V}$

$$\therefore \frac{dv_L}{dt} = 25,000(2 \cos 400t - \sin 400t)e^{-200t} \text{ V/s}$$

$$\frac{dv_L}{dt} = 0 \quad \text{when} \quad \tan 400t = 2$$

$$\therefore t = 2.77 \text{ ms}$$

Also  $400t = 1.107 + \pi$  etc.

Because of the decaying exponential  $v_L$  will be maximum the first time the derivative is zero.

[b]  $v_L(\text{max}) = [125 \sin 1.107]e^{-0.554} = 64.27 \text{ V}$

$$v_L \text{ max} = 64.27 \text{ V}$$

Note: When  $t = (1.107 + \pi)/400$ ;  $v_L = -13.36 \text{ V}$

P 5.10 [a]  $i = \frac{1000}{50} \int_0^t 250 \sin 1000x \, dx - 5$

$$= 5000 \int_0^t \sin 1000x \, dx - 5$$

$$= 5000 \left[ \frac{-\cos 1000x}{1000} \right]_0^t - 5$$

$$= 5(1 - \cos 1000t) - 5$$

$$i = -5 \cos 1000t \text{ A}$$

[b]  $p = vi = (250 \sin 1000t)(-5 \cos 1000t)$

$$= -1250 \sin 1000t \cos 1000t$$





$$p = -625 \sin 2000t \text{ W}$$

$$w = \frac{1}{2} Li^2$$

$$= \frac{1}{2} (50 \times 10^{-3}) 25 \cos^2 1000t$$

$$= 625 \cos^2 1000t \text{ mJ}$$
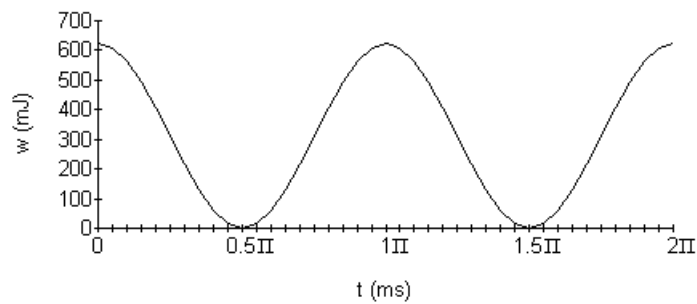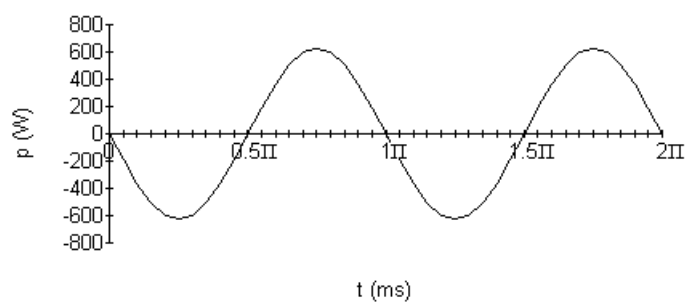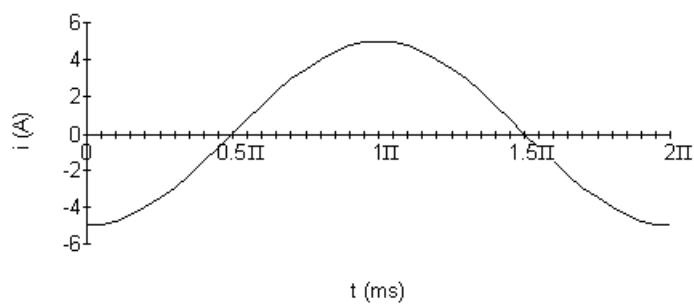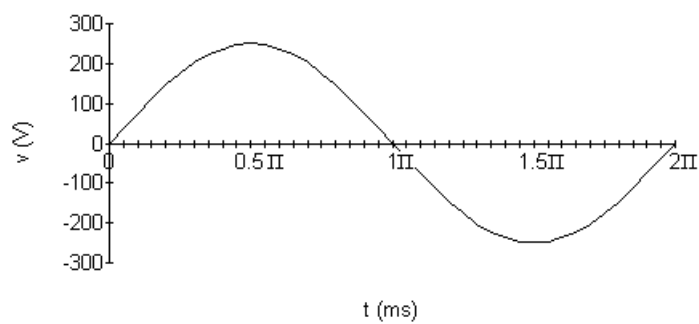
$$w = [312.5 + 312.5 \cos 2000t] \text{ mJ.}$$





[c]	Absorbing power:	Delivering power:
	$0.5\pi \leq t \leq \pi \text{ ms}$	$0 \leq t \leq 0.5\pi \text{ ms}$
	$1.5\pi \leq t \leq 2\pi \text{ ms}$	$\pi \leq t \leq 1.5\pi \text{ ms}$

P 5.11  $i = (B_1 \cos 5t + B_2 \sin 5t)e^{-t}$

$$i(0) = B_1 = 25 \text{ A}$$

$$\begin{aligned} \frac{di}{dt} &= (B_1 \cos 5t + B_2 \sin 5t)(-e^{-t}) + e^{-t}(-5B_1 \sin 5t + 5B_2 \cos 5t) \\ &= [(5B_2 - B_1) \cos 5t - (5B_1 + B_2) \sin 5t]e^{-t} \end{aligned}$$

$$v = 2 \frac{di}{dt} = [(10B_2 - 2B_1) \cos 5t - (10B_1 + 2B_2) \sin 5t]e^{-t}$$

$$v(0) = 100 = 10B_2 - 2B_1 = 10B_2 - 50 \quad \therefore \quad B_2 = 150/10 = 15 \text{ A}$$

Thus,

$$i = (25 \cos 5t + 15 \sin 5t)e^{-t} \text{ A}, \quad t \geq 0$$

$$v = (100 \cos 5t - 280 \sin 5t)e^{-t} \text{ V}, \quad t \geq 0$$

$$i(0.5) = -6.70 \text{ A}; \quad v(0.5) = -150.23 \text{ V}$$

$$p(0.5) = (-6.70)(-150.23) = 1007.00 \text{ W absorbing}$$

P 5.12 [a]  $v(20 \mu\text{s}) = 12.5 \times 10^9 (20 \times 10^{-6})^2 = 5 \text{ V}$  (end of first interval)

$$\begin{aligned} v(20 \mu\text{s}) &= 10^6 (20 \times 10^{-6}) - (12.5)(400) \times 10^{-3} - 10 \\ &= 5 \text{ V (start of second interval)} \end{aligned}$$

$$\begin{aligned} v(40 \mu\text{s}) &= 10^6 (40 \times 10^{-6}) - (12.5)(1600) \times 10^{-3} - 10 \\ &= 10 \text{ V (end of second interval)} \end{aligned}$$

[b]  $p(10 \mu\text{s}) = 62.5 \times 10^{12} (10^{-5})^3 = 62.5 \text{ mW}, \quad v(10 \mu\text{s}) = 1.25 \text{ V},$

$$i(10 \mu\text{s}) = 50 \text{ mA}, \quad p(10 \mu\text{s}) = vi = 62.5 \text{ mW},$$

$$p(30 \mu\text{s}) = 437.50 \text{ mW}, \quad v(30 \mu\text{s}) = 8.75 \text{ V}, \quad i(30 \mu\text{s}) = 0.05 \text{ A}$$

$$[\mathbf{c}] \quad w(10 \mu\text{s}) = 15.625 \times 10^{12} (10 \times 10^{-6})^4 = 0.15625 \mu\text{J}$$

$$w = 0.5 C v^2 = 0.5 (0.2 \times 10^{-6}) (1.25)^2 = 0.15625 \mu\text{J}$$

$$w(30 \mu\text{s}) = 7.65625 \mu\text{J}$$

$$w(30 \mu\text{s}) = 0.5 (0.2 \times 10^{-6}) (8.75)^2 = 7.65625 \mu\text{J}$$

P 5.13    **[a]**  $0 \leq t \leq 50 \mu\text{s}$

$$C = 0.5 \mu\text{F} \quad \frac{1}{C} = 2 \times 10^6$$

$$v = 2 \times 10^6 \int_0^t 20 \times 10^{-3} dx + 20$$

$$v = 40 \times 10^3 t + 20 \text{ V} \quad 0 \leq t \leq 50 \mu\text{s}$$

$$v(50 \mu\text{s}) = 2 + 20 = 22 \text{ V}$$

**[b]**  $50 \mu\text{s} \leq t \leq 200 \mu\text{s}$

$$v = 2 \times 10^6 \int_{50 \times 10^{-6}}^t -40 \times 10^{-3} dx + 22 = -8 \times 10^4 t + 4 + 22$$


$$v = -8 \times 10^4 t + 26 \text{ V} \quad 50 \leq t \leq 200 \mu\text{s}$$

$$v(200 \mu\text{s}) = -8 \times 10^4 (200 \times 10^{-6}) + 26 = 10 \text{ V}$$

**[c]**  $200 \leq t \leq \infty$

$$v = 2 \times 10^6 \int_{200 \times 10^{-6}}^t 0 dx + 10 = 10 \text{ V} \quad 200 \mu\text{s} \leq t \leq \infty$$

**[d]**

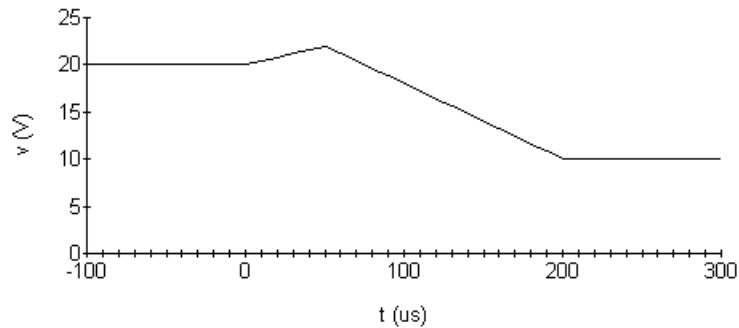

P 5.14     $i_C = C(dv/dt)$

$0 < t < 1:$


$$v_c = 20t^3 \text{ V}$$

$$i_C = 0.8 \times 10^{-6} (60)t^2 = 48t^2 \mu\text{A}$$

$1 < t < 3:$

$$v_c = 2.5(3 - t)^3 \text{ V}$$
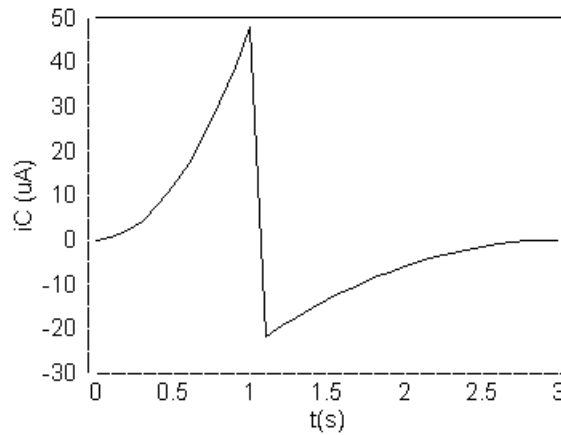
$$i_C = 0.8 \times 10^{-6}(7.5)(3 - t)^2(-1) = -6(3 - t)^2 \mu\text{A}$$



P 5.15 [a]  $v = 5 \times 10^6 \int_0^{250 \times 10^{-6}} 100 \times 10^{-3} e^{-1000t} dt - 60.6$

$$= 500 \times 10^3 \frac{e^{-1000t}}{-1000} \Big|_0^{250 \times 10^{-6}} - 60.6$$

$$= 500(1 - e^{-0.25}) - 60.6 = 50 \text{ V}$$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.2)(10^{-6})(50)^2 = 250 \mu\text{J}$$

[b]  $v = 500 - 60.6 = 439.40 \text{ V}$

$$w = \frac{1}{2} (0.2) \times 10^{-6} (439.40)^2 = 19.31 \text{ mJ} = 19,307.24 \mu\text{J}$$

P 5.16 [a]  $w(0) = \frac{1}{2} C [v(0)]^2 = \frac{1}{2} (0.40) \times 10^{-6} (25)^2 = 125 \mu\text{J}$

[b]  $v = (A_1 t + A_2) e^{-1500t} \quad v(0) = A_2 = 25 \text{ V}$

$$\frac{dv}{dt} = -1500 e^{-1500t} (A_1 t + A_2) + e^{-1500t} (A_1)$$

$$= (-1500 A_1 t - 1500 A_2 + A_1) e^{-1500t}$$

$$\frac{dv}{dt}(0) = A_1 - 1500 A_2, \quad i = C \frac{dv}{dt}, \quad i(0) = C \frac{dv(0)}{dt}$$

$$\therefore \frac{dv(0)}{dt} = \frac{i(0)}{C} = \frac{90 \times 10^{-3}}{0.40 \times 10^{-6}} = 225 \times 10^3$$

$$\therefore 225 \times 10^3 = A_1 - 1500(25)$$

$$\text{Thus, } A_1 = 2.25 \times 10^5 + 3.75 \times 10^4 = 262,500 \frac{\text{V}}{\text{s}}$$

$$[\mathbf{c}] \quad v = (262,500t + 25)e^{-1500t}$$

$$i = C \frac{dv}{dt} = 0.40 \times 10^{-6} \frac{d}{dt}(262,500t + 25)e^{-1500t}$$

$$i = \frac{d}{dt} [(0.105t + 10 \times 10^{-6})e^{-1500t}]$$

$$= (0.105t + 10 \times 10^{-6})(-1500)e^{-1500t} + e^{-1500t}(0.105)$$

$$= (-157.5t - 15 \times 10^{-3} + 0.105)e^{-1500t}$$

$$= (0.09 - 157.5t)e^{-1500t} \text{ A}, \quad t \geq 0$$

$$= (90 - 157,500t)e^{-1500t} \text{ mA}, \quad t \geq 0$$

$$\text{P 5.17} \quad [\mathbf{a}] \quad i = \frac{50 \times 10^{-3}}{10 \times 10^{-6}}t = 5 \times 10^3 t \quad 0 \leq t \leq 10 \mu\text{s}$$

$$i = 50 \times 10^{-3} \quad 10 \leq t \leq 30 \mu\text{s}$$

$$q = \int_0^{10 \times 10^{-6}} 5 \times 10^3 t \, dt + \int_{10 \times 10^{-6}}^{30 \times 10^{-6}} 50 \times 10^{-3} \, dt$$

$$= 5 \times 10^3 \frac{t^2}{2} \Big|_0^{10 \times 10^{-6}} + 50 \times 10^{-3} (20 \times 10^{-6})$$

$$= 5 \times 10^3 \left(\frac{1}{2}\right) (100 \times 10^{-12}) + 1000 \times 10^{-3} \times 10^{-6}$$

$$= 1.25 \mu\text{C}$$

$$[\mathbf{b}] \quad i = 200 \times 10^{-3} - 5 \times 10^{-3}t \quad 30 \mu\text{s} \leq t \leq 50 \mu\text{s}$$

$$q = 1.25 \times 10^{-6} + \int_{30 \times 10^{-6}}^{50 \times 10^{-6}} [200 \times 10^{-3} - 5 \times 10^3 t] \, dt$$

$$= 1.25 \times 10^{-6} + 200 \times 10^{-3} (20 \times 10^{-6}) - 5 \times 10^3 \frac{t^2}{2} \Big|_{30 \times 10^{-6}}^{50 \times 10^{-6}}$$

$$= 1.25 \times 10^{-6} + 4000 \times 10^{-9} - 5 \times 10^3 \left[ \frac{2500 - 900}{2} \right] 10^{-12}$$

$$= 1.25 \mu\text{C}$$

$$\text{Since } q = vC, \quad \therefore v = 1.25/0.25 = 5 \text{ V.}$$

$$[\mathbf{c}] \quad i = -300 \times 10^{-3} + 5 \times 10^{-3}t \quad 50 \mu\text{s} \leq t \leq 60 \mu\text{s}$$

$$\begin{aligned}
q &= 1.25 \times 10^{-6} + \int_{50 \times 10^{-6}}^{60 \times 10^{-6}} [-300 \times 10^{-3} + 5 \times 10^3 t] dt \\
&= 1.25 \times 10^{-6} - 300 \times 10^{-3}(10 \times 10^{-6}) + 5 \times 10^3 \left[ \frac{3600 - 2500}{2} \right] 10^{-12} \\
&= 1 \mu\text{C} \\
v &= \frac{1 \times 10^{-6}}{0.25 \times 10^{-6}} = 4 \text{ V} \\
w &= \frac{C}{2} v^2 = \frac{1}{2} (0.25) \times 10^{-6} (16) = 2 \mu\text{J}
\end{aligned}$$

P 5.18  $v = -60 \text{ V}, \quad t \leq 0; \quad C = 0.4 \mu\text{F}$

$$v = 15 - 15e^{-500t}(5 \cos 2000t + \sin 2000t) \text{ V}, \quad t \geq 0$$

[a]  $i = 0, \quad t < 0$

$$\begin{aligned}
\text{[b]} \quad \frac{dv}{dt} &= -15[(5 \cos 2000t + \sin 2000t)(-500e^{-500t}) + \\
&\quad (e^{-500t})(-10,000 \sin 2000t + 2000 \cos 2000t)] \\
&= 15e^{-500t}(500 \cos 2000t + 10,500 \sin 2000t) \\
i &= C \frac{dv}{dt} = 0.4 \times 10^{-6} (7500)e^{-500t}(\cos 2000t + 21 \sin 2000t) \\
&= 3e^{-500t}(\cos 2000t + 21 \sin 2000t) \text{ mA}, \quad t > 0
\end{aligned}$$

[c] no

[d] yes, from 0 to 3 mA

[e]  $v(\infty) = 15 \text{ V}$

$$w = \frac{1}{2} C v^2 = \frac{1}{2} (0.4) 225 \times 10^{-6} = 45 \mu\text{J}$$

P 5.19  $10 \parallel (15 + 25) = 8 \text{ H}$

$$8 \parallel 12 = 4.8 \text{ H}$$

$$44 \parallel (1.2 + 4.8) = 5.28 \text{ H}$$

$$21 \parallel 4 = 3.36 \text{ H}$$

$$5.28 + 3.36 = 8.64 \text{ H}$$

P 5.20  $6 \parallel 14 = 4.2 \text{ H}$

$$15.8 + 4.2 = 20 \text{ H}$$

$$20 \parallel 60 = 15 \text{ H}$$

$$15 + 5 = 20 \text{ H}$$

$$20 \parallel 80 = 16 \text{ H}$$

$$16 + 24 = 40 \text{ H}$$

$$40 \parallel 10 = 8 \text{ H}$$

$$L_{ab} = 12 + 8 = 20 \text{ H}$$

P 5.21 From Figure 5.17(a) we have

$$v = \frac{1}{C_1} \int_0^t i + v_1(0) + \frac{1}{C_2} \int_0^t i dx + v_2(0) + \cdots$$

$$v = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \cdots \right] \int_0^t i dx + v_1(0) + v_2(0) + \cdots$$


$$\text{Therefore } \frac{1}{C_{\text{eq}}} = \left[ \frac{1}{C_1} + \frac{1}{C_2} + \cdots \right], \quad v_{\text{eq}}(0) = v_1(0) + v_2(0) + \cdots$$

P 5.22 From Fig. 5.18(a)


$$i = C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \cdots = [C_1 + C_2 + \cdots] \frac{dv}{dt}$$

Therefore  $C_{\text{eq}} = C_1 + C_2 + \cdots$ . Because the capacitors are in parallel, the initial voltage on every capacitor must be the same. This initial voltage would appear on  $C_{\text{eq}}$ .

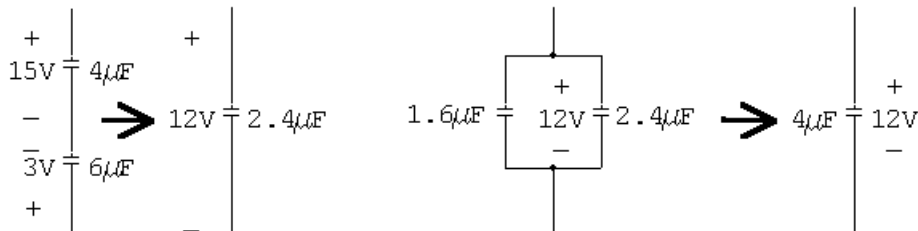
P 5.23  $\frac{1}{4} + \frac{1}{6} = \frac{5}{12} \quad \therefore C_{\text{eq}} = 2.4 \mu\text{F}$


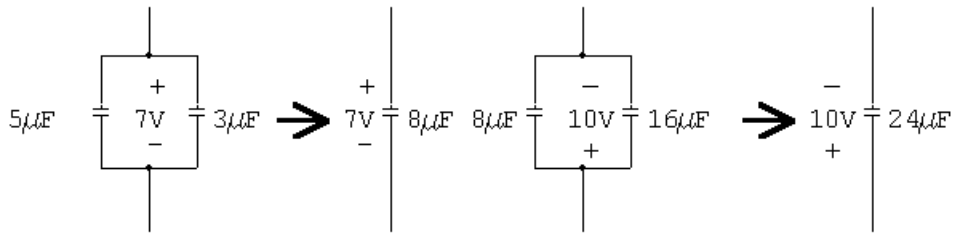
$$\frac{1}{4} + \frac{1}{12} = \frac{4}{12} \quad \therefore C_{\text{eq}} = 3 \mu\text{F}$$



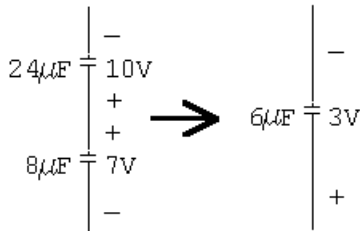
$$\frac{1}{24} + \frac{1}{8} = \frac{4}{24} \quad \therefore C_{\text{eq}} = 6 \mu\text{F}$$





P 5.24  $\frac{1}{C_1} = \frac{1}{8} + \frac{1}{32} = \frac{5}{32}; \quad C_1 = 6.4 \text{ nF}$

$$C_2 = 5.6 + 6.4 = 12 \text{ nF}$$

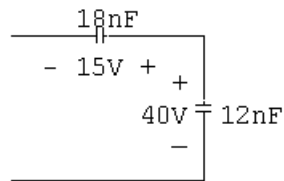


$$\frac{1}{C_3} = \frac{1}{18} + \frac{1}{12} = \frac{10}{72}; \quad C_3 = 7.2 \text{ nF}$$

$$C_4 = 12.8 + 7.2 = 20 \text{ nF}$$

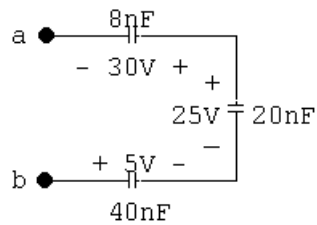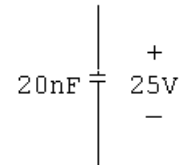

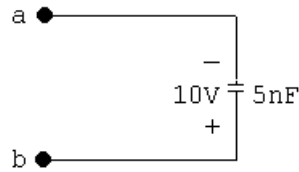
$$\frac{1}{C_5} = \frac{1}{8} + \frac{1}{20} + \frac{1}{40} = \frac{1}{5}; \quad C_5 = 5 \text{ nF}$$




P 5.25 [a]  $i_o(0) = i_1(0) + i_2(0) = 5 \text{ A}$

[b]

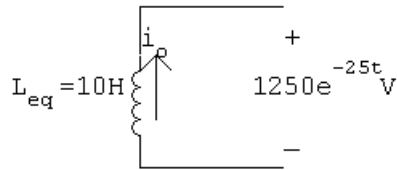

$$\begin{aligned} i_o &= -\frac{1}{10} \int_0^t 1250e^{-25x} dx + 5 = -125 \left[ \frac{e^{-25x}}{-25} \right]_0^t + 5 \\ &= 5(e^{-25t} - 1) + 5 = 5e^{-25t} \text{ A}, \quad t \geq 0 \end{aligned}$$

[c]

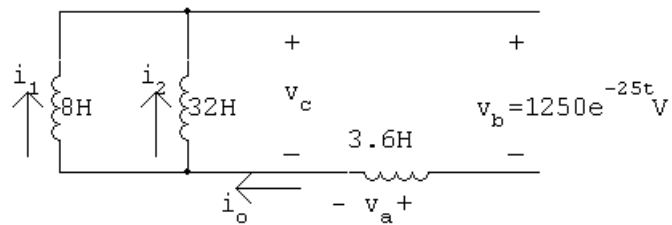

$$v_a = 3.6 \frac{d}{dt} (5e^{-25t}) = -450e^{-25t} \text{ V}$$

$$\begin{aligned} v_c &= v_a + v_b = -450e^{-25t} + 1250e^{-25t} \\ &= 800e^{-25t} \text{ V} \end{aligned}$$

$$i_1 = -\frac{1}{8} \int_0^t 800e^{-25x} dx + 10$$

$$= 4e^{-25t} - 4 + 10$$

$$i_1 = 4e^{-25t} + 6 \text{ A} \quad t \geq 0$$

[d]  $i_2 = -\frac{1}{32} \int_0^t 800e^{-25x} dx - 5$

$$= e^{-25t} - 1 - 5$$

$$i_2 = e^{-25t} - 6 \text{ A}, \quad t \geq 0$$



$$[\mathbf{e}] \quad w(0) = \frac{1}{2}(8)(100) + \frac{1}{2}(32)(25) + \frac{1}{2}(3.6)(25) = 845 \text{ J}$$

$$[\mathbf{f}] \quad w_{\text{del}} = \frac{1}{2}(10)(25) = 125 \text{ J}$$

$$[\mathbf{g}] \quad w_{\text{trapped}} = 845 - 125 = 720 \text{ J}$$

$$\text{P 5.26} \quad v_{\text{b}} = 1250e^{-25t} \text{ V}$$

$$i_{\text{o}} = 5e^{-25t} \text{ A}$$

$$p = 6250e^{-50t} \text{ W}$$

$$w = \int_0^t 6250e^{-50x} dx = 6250 \frac{e^{-50x}}{-50} \bigg|_0^t = 125(1 - e^{-50t}) \text{ W}$$


$$w_{\text{total}} = 125 \text{ J}$$

$$80\%w_{\text{total}} = 100 \text{ J}$$

Thus,

$$125 - 125e^{-50t} = 100; \quad e^{50t} = 5; \quad \therefore t = 32.19 \text{ ms}$$

$$\text{P 5.27} \quad [\mathbf{a}]$$

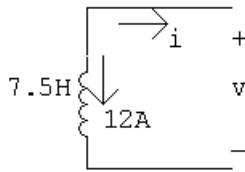

$$i(t) = -\frac{1}{7.5} \int_0^t -1800e^{-20x} dx - 12$$

$$= 240 \frac{e^{-20x}}{-20} \bigg|_0^t - 12$$

$$= -12(e^{-20t} - 1) - 12$$

$$i(t) = -12e^{-20t} \text{ A}$$

$$[\mathbf{b}] \quad i_1(t) = -\frac{1}{10} \int_0^t -1800e^{-20x} dx + 4$$

$$= 180 \frac{e^{-20x}}{-20} \bigg|_0^t + 4$$

$$= -9(e^{-20t} - 1) + 4$$

$$i_1(t) = -9e^{-20t} + 13 \text{ A}$$

$$[\mathbf{c}] \quad i_2(t) = -\frac{1}{30} \int_0^t -1800e^{-20x} dx - 16$$

$$= 60 \frac{e^{-20x}}{-20} \Big|_0^t - 16$$

$$= -3(e^{-20t} - 1) - 16$$

$$i_2(t) = -3e^{-20t} - 13 \text{ A}$$

$$[\mathbf{d}] \quad p = vi = (-1800e^{-20t})(-12e^{-20t}) = 21,600e^{-40t} \text{ W}$$

$$w = \int_0^\infty p dt = \int_0^\infty 21,600e^{-40t} dt$$

$$= 21,600 \frac{e^{-40t}}{-40} \Big|_0^\infty$$

$$= 540 \text{ J}$$


$$[\mathbf{e}] \quad w = \frac{1}{2}(10)(16) + \frac{1}{2}(30)(256) = 3920 \text{ J}$$

$$[\mathbf{f}] \quad w_{\text{trapped}} = \frac{1}{2}(10)(13)^2 + \frac{1}{2}(30)(13)^2 = 3380 \text{ J}$$

$$w_{\text{trapped}} = 3920 - 540 = 3380 \text{ J} \quad \text{checks}$$

[\mathbf{g}] Yes, they agree.

P 5.28 [\mathbf{a}]

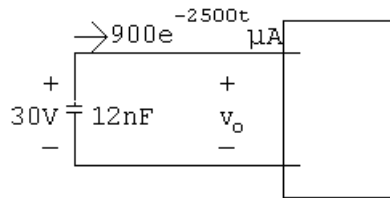

$$v_o = -\frac{10^9}{12} \int_0^t 900 \times 10^{-6} e^{-2500x} dx + 30$$

$$= -75,000 \frac{e^{-2500x}}{-2500} \Big|_0^t + 30$$

$$= 30e^{-2500t} \text{ V}, \quad t \geq 0$$

$$[\mathbf{b}] \quad v_1 = -\frac{10^9}{20} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t + 45$$

$$= 18e^{-2500t} + 27 \text{ V}, \quad t \geq 0$$

$$[\mathbf{c}] \quad v_2 = -\frac{10^9}{30} (900 \times 10^{-6}) \frac{e^{-2500x}}{-2500} \Big|_0^t - 15$$

$$= 12e^{-2500t} - 27 \text{ V}, \quad t \geq 0$$

$$\begin{aligned}
[\text{d}] \quad p &= vi = (30e^{-2500t})(900 \times 10^{-6})e^{-2500t} \\
&= 27 \times 10^{-3}e^{-5000t} \\
w &= \int_0^\infty 27 \times 10^{-3}e^{-5000t} dt \\
&= 27 \times 10^{-3} \left. \frac{e^{-5000t}}{-5000} \right|_0^\infty \\
&= -5.4 \times 10^{-6}(0 - 1) = 5.4 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
[\text{e}] \quad w &= \frac{1}{2}(20 \times 10^{-9})(45)^2 + \frac{1}{2}(30 \times 10^{-9})(15)^2 \\
&= 20.25 \times 10^{-6} + 3.375 \times 10^{-6} \\
&= 23.625 \mu\text{J}
\end{aligned}$$

$$\begin{aligned}
[\text{f}] \quad w_{\text{trapped}} &= \frac{1}{2}(20 \times 10^{-9})(27)^2 + \frac{1}{2}(30 \times 10^{-9})(27)^2 \\
&= (10 + 15)(27)^2 \times 10^{-9} \\
&= 18.225 \mu\text{J}
\end{aligned}$$

$$\text{CHECK: } 18.225 + 5.4 = 23.625 \mu\text{J}$$

[g] Yes, they agree.


$$\text{P 5.29} \quad C_1 = 1 + 1.5 = 2.5 \text{ nF}$$

$$\frac{1}{C_2} = \frac{1}{2.5} + \frac{1}{12.5} + \frac{1}{50} = \frac{1}{2}$$

$$\therefore C_2 = 2 \text{ nF}$$

$$v_d(0) + v_a(0) - v_c(0) = 40 + 15 + 45 = 100 \text{ V}$$

[a]

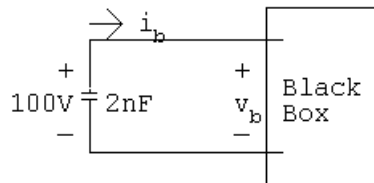

$$\begin{aligned}
v_b &= -\frac{10^9}{2} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 100 \\
&= -25,000 \left. \frac{e^{-250x}}{-250} \right|_0^t + 100 \\
&= 100(e^{-250t} - 1) + 100 \\
&= 100e^{-250t} \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
[\mathbf{b}] \quad v_a &= -\frac{10^9}{12.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 15 \\
&= -4000 \frac{e^{-250x}}{-250} \Big|_0^t + 15 \\
&= 16(e^{-250t} - 1) + 15 \\
&= 16e^{-250t} - 1 \text{ V}
\end{aligned}$$

$$\begin{aligned}
[\mathbf{c}] \quad v_c &= \frac{10^9}{50} \int_0^t 50 \times 10^{-6} e^{-250x} dx - 45 \\
&= 1000 \frac{e^{-250x}}{-250} \Big|_0^t - 45 \\
&= -4(e^{-250t} - 1) - 45 \\
&= -4e^{-250t} - 41 \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
[\mathbf{d}] \quad v_d &= -\frac{10^9}{2.5} \int_0^t 50 \times 10^{-6} e^{-250x} dx + 40 \\
&= -20,000 \frac{e^{-250x}}{-250} \Big|_0^t + 40 \\
&= 80(e^{-250t} - 1) + 40 \\
&= 80e^{-250t} - 40 \text{ V}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
\text{CHECK: } v_b &= v_d + v_a - v_c \\
&= 80e^{-250t} - 40 + 16e^{-250t} - 1 + 4e^{-250t} + 41 \\
&= 100e^{-250t} \text{ V} \quad (\text{checks})
\end{aligned}$$

$$\begin{aligned}
[\mathbf{e}] \quad i_1 &= -10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -10^{-9} (-20,000e^{-250t}) \\
&= 20e^{-250t} \mu\text{A}, \quad t \geq 0
\end{aligned}$$

$$\begin{aligned}
[\mathbf{f}] \quad i_2 &= -1.5 \times 10^{-9} \frac{d}{dt} [80e^{-250t} - 40] \\
&= -1.5 \times 10^{-9} (-20,000e^{-250t}) \\
&= 30e^{-250t} \mu\text{A}, \quad t \geq 0
\end{aligned}$$

$$\text{CHECK: } i_1 + i_2 = 50e^{-250t} \mu\text{A} = i_b$$

$$\begin{aligned}\text{P 5.30 [a]} \quad w(0) &= \left[ \frac{1}{2}(2.5)(40)^2 + \frac{1}{2}(12.5)(15)^2 + \frac{1}{2}(50)(45)^2 \right] \times 10^{-9} \\ &= 54,031.25 \text{ nJ}\end{aligned}$$

$$\text{[b]} \quad v_a(\infty) = -1 \text{ V}$$

$$v_c(\infty) = -41 \text{ V}$$

$$v_d(\infty) = -40 \text{ V}$$

$$\begin{aligned}w(\infty) &= \left[ \frac{1}{2}(2.5)(40)^2 + \frac{1}{2}(12.5)(1)^2 + \frac{1}{2}(50)(41)^2 \right] \times 10^{-9} \\ &= 44,031.25 \text{ nJ}\end{aligned}$$

$$\begin{aligned}\text{[c]} \quad w &= \int_0^\infty (100e^{-250t})(50e^{-250t}) \times 10^{-6} dt = 10,000 \text{ nJ} \\ \text{CHECK: } &54,031.25 - 44,031.25 = 10,000\end{aligned}$$

$$\text{[d]} \quad \% \text{ delivered} = \frac{10,000}{54,031.25} \times 100 = 18.51\%$$

$$\text{[e]} \quad w = 5 \times 10^{-3} \int_0^t e^{-500x} dx$$

$$= 10^4(1 - e^{-500t}) \text{ nJ}$$

$$\therefore 10^4(1 - e^{-500t}) = 5000; \quad e^{-500t} = 0.5$$

$$\text{Thus, } t = (\ln 2)/500 = 1.39 \text{ ms.}$$

$$\text{P 5.31 [a]} \quad \frac{v}{i} = R = \frac{100e^{-80t}}{4e^{-80t}} = 25 \Omega$$

$$\text{[b]} \quad \tau = \frac{1}{80} = 12.5 \text{ ms}$$

$$\text{[c]} \quad \tau = \frac{L}{R} = 12.5 \times 10^{-3}$$

$$L = (12.5)(25) \times 10^{-3} = 312.5 \text{ mH}$$

$$\text{[d]} \quad w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(0.3125)(16) = 2.5 \text{ J}$$


$$\text{[e]} \quad w_{\text{diss}} = \int_0^t 400e^{-160x} dx = 2.5 - 2.5e^{-160t}$$

$$0.8w(0) = (0.8)(2.5) = 2 \text{ J}$$

$$2.5 - 2.5e^{-160t} = 2 \quad \therefore e^{-160t} = 0.5$$


$$\text{Solving, } t = 10.06 \text{ ms.}$$

P 5.32 [a]  $t < 0$  :

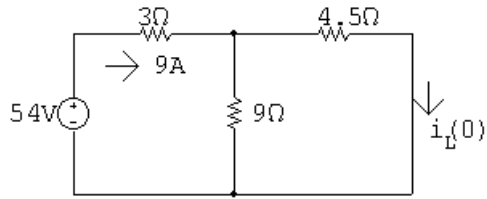

$$\frac{(9)(4.5)}{13.5} = 3\Omega; \quad i_L(0) = 9 \frac{9}{13.5} = 6\text{ A}$$


$t > 0$ :

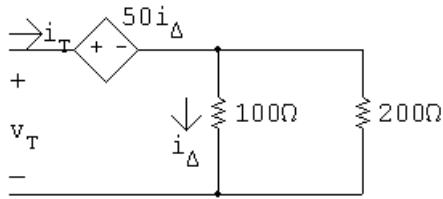

$$i_\Delta = \frac{i_T(200)}{300} = \frac{2}{3}i_T$$

$$v_T = 50i_\Delta + i_T \frac{(100)(200)}{300} = 50i_T \frac{2}{3} + \frac{200}{3}i_T$$
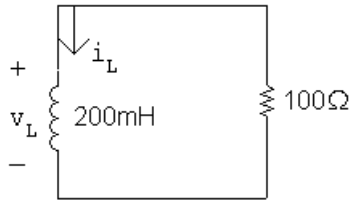
$$\frac{v_T}{i_T} = R_{Th} = \frac{100}{3} + \frac{200}{3} = 100\Omega$$




$$\tau = \frac{L}{R} = \frac{200}{100} \times 10^{-3} \quad \frac{1}{\tau} = 500$$

$$i_L = 6e^{-500t} \text{ A}, \quad t \geq 0$$

[b]  $v_L = 200 \times 10^{-3}(-3000e^{-500t}) = -600e^{-500t} \text{ V}, \quad t \geq 0^+$

[c]

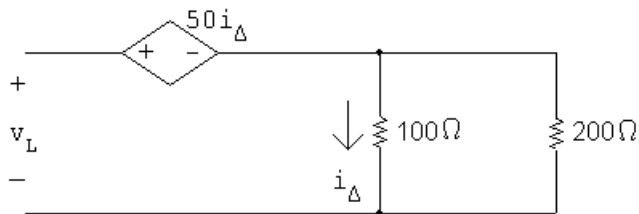

$$v_L = 50i_\Delta + 100i_\Delta = 150i_\Delta$$

$$i_{\Delta} = \frac{v_L}{150} = -4e^{-500t} \text{ A} \quad t \geq 0^+$$

P 5.33  $w(0) = \frac{1}{2}(200 \times 10^{-3})(36) = 3.6 \text{ J}$

$$p_{50i_{\Delta}} = -50i_{\Delta}i_L = -50(-4e^{-500t})(6e^{-500t}) = 1200e^{-1000t} \text{ W}$$

$$w_{50i_{\Delta}} = \int_0^{\infty} 1200e^{-1000t} dt = 1200 \frac{e^{-1000t}}{-1000} \Big|_0^{\infty} = 1.2 \text{ J}$$

$$\% \text{ dissipated} = \frac{1.2}{3.6}(100) = 33.33\%$$

P 5.34 [a]  $i(0) = 125/25 = 5 \text{ A}$

[b]  $\tau = \frac{L}{R} = \frac{4}{100} = 40 \text{ ms}$

[c]  $i = 5e^{-25t} \text{ A}, \quad t \geq 0$

$$v_1 = L \frac{di_1}{dt} = 4(-125e^{-25t}) = -500e^{-25t} \text{ V} \quad t \geq 0^+$$

$$v_2 = -80i = -400e^{-25t} \text{ V} \quad t \geq 0$$

[d]  $p_{\text{diss}} = i^2(20) = 25e^{-50t}(20) = 500e^{-50t} \text{ W}$


$$w_{\text{diss}} = \int_0^t 500e^{-50x} dx = 500 \frac{e^{-50x}}{-50} \Big|_0^t = 10 - 10e^{-50t} \text{ J}$$

$$w_{\text{diss}}(12 \text{ ms}) = 10 - 10e^{-0.6} = 4.51 \text{ J}$$

$$w(0) = \frac{1}{2}(4)(25) = 50 \text{ J}$$

$$\% \text{ dissipated} = \frac{4.51}{50}(100) = 9.02\%$$


P 5.35 [a]  $t < 0$

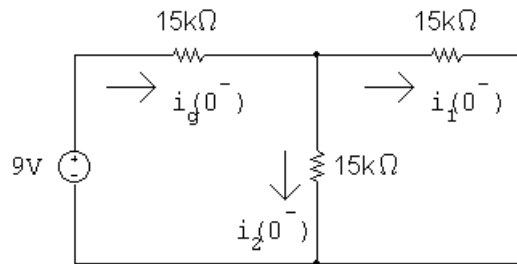

$$15 \text{ k}\Omega \parallel 15 \text{ k}\Omega = 7.5 \text{ k}\Omega$$

$$i_g(0^-) = \frac{9}{(15 + 7.5) \times 10^3} = 0.4 \text{ mA}$$
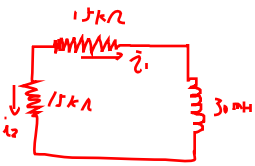
$$i_1(0^-) = i_2(0^-) = (0.4 \times 10^{-3}) \frac{(15)}{(30)} = 0.2 \text{ mA}$$



[b]  $i_1(0^+) = i_1(0^-) = 0.2 \text{ mA}$

$i_2(0^+) = -i_1(0^+) = -0.2 \text{ mA}$  (when switch is open)

[c]  $\tau = \frac{L}{R} = \frac{30 \times 10^{-3}}{30 \times 10^3} = 10^{-6}; \quad \frac{1}{\tau} = 10^6$

$i_1(t) = i_1(0^+)e^{-t/\tau}$


$i_1(t) = 0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0$

[d]  $i_2(t) = -i_1(t)$  when  $t \geq 0^+$

$\therefore i_2(t) = -0.2e^{-10^6 t} \text{ mA}, \quad t \geq 0^+$

[e] The current in a resistor can change instantaneously. The switching operation forces  $i_2(0^-)$  to equal  $0.2 \text{ mA}$  and  $i_2(0^+) = -0.2 \text{ mA}$ .


P 5.36 [a] For  $t < 0$

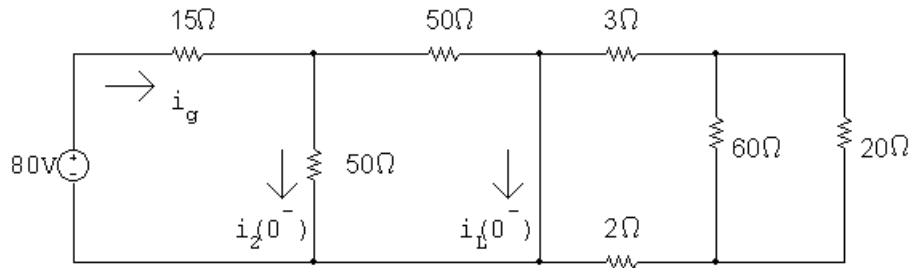

$i_g = \frac{80}{40} = 2 \text{ A}$

$i_L(0^-) = \frac{2(50)}{(100)} = 1 \text{ A} = i_L(0^+)$

For  $t > 0$

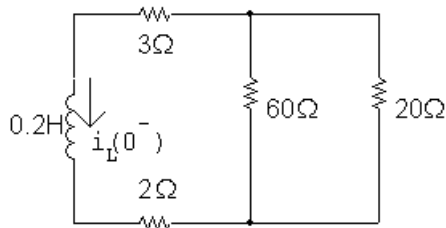

$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$

$\tau = \frac{L}{R} = \frac{0.20}{5 + 15} = \frac{1}{100} = 0.01 \text{ s}$

$i_L(0^+) = 1 \text{ A}$



$$i_L(t) = e^{-100t} \text{ A}, \quad t \geq 0$$

$$v_o(t) = -15i_L(t)$$

$$v_o(t) = -15e^{-100t} \text{ V}, \quad t \geq 0^+$$

P 5.37  $P_{20\Omega} = \frac{v_o^2}{20} = 11.25e^{-200t} \text{ W}$


$$w_{\text{diss}} = \int_0^{0.01} 11.25e^{-200t} dt$$


$$= \frac{11.25}{-200} e^{-200t} \Big|_0^{0.01}$$

$$= 56.25 \times 10^{-3} (1 - e^{-2}) = 48.64 \text{ mJ}$$


$$w_{\text{stored}} = \frac{1}{2} (0.2)(1)^2 = 100 \text{ mJ}.$$


$$\% \text{ diss} = \frac{48.64}{100} \times 100 = 48.64\%$$

P 5.38  $t < 0$   

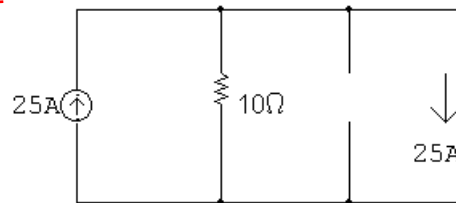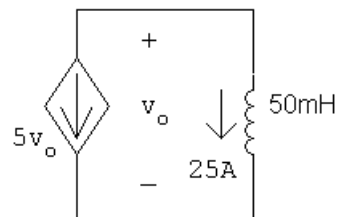
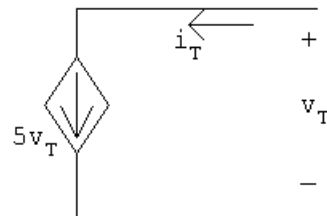


$$i_L(0^-) = i_L(0^+) = 25 \text{ A}$$

$t > 0$   


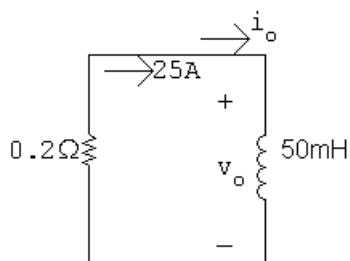


Find Thévenin resistance seen by inductor



$$i_T = 5v_T; \quad \frac{v_T}{i_T} = R_{\text{Th}} = \frac{1}{5} = 0.2 \Omega$$


$$\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{0.2} = 250 \text{ ms}; \quad 1/\tau = 4$$




$$i_o = 25e^{-4t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (50 \times 10^{-3})(-100e^{-4t}) = -5e^{-4t} \text{ V}, \quad t \geq 0^+$$

P 5.39 [a]  $t < 0$  :

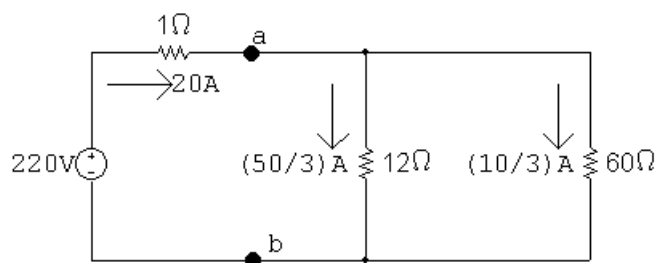


$t = 0^+$ :

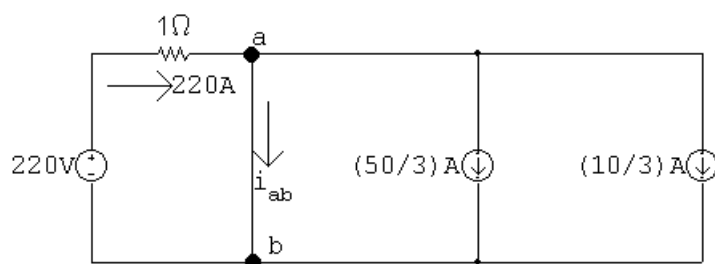


$$220 = i_{ab} + (50/3) + (10/3), \quad i_{ab} = 200 \text{ A}, \quad t = 0^+$$

[b] At  $t = \infty$ :

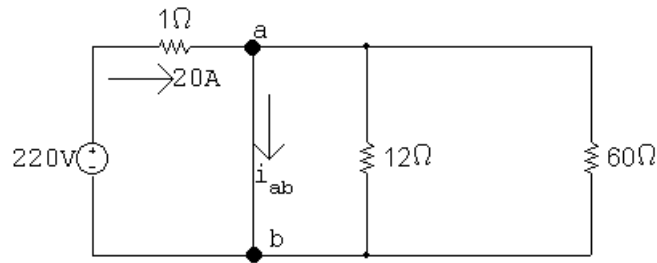
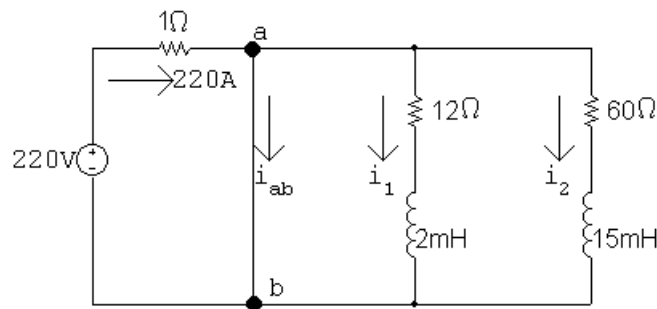
$$i_{ab} = 220/1 = 220 \text{ A}, \quad t = \infty$$



[c]  $i_1(0) = 50/3, \quad \tau_1 = \frac{2}{12} \times 10^{-3} = 0.167 \text{ ms}$

$$i_2(0) = 10/3, \quad \tau_2 = \frac{15}{60} \times 10^{-3} = 0.25 \text{ ms}$$

$$i_1(t) = (50/3)e^{-6000t} \text{ A}, \quad t \geq 0$$

$$i_2(t) = (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} \text{ A}, \quad t \geq 0$$

$$220 - (50/3)e^{-6000t} - (10/3)e^{-4000t} = 210$$

$$30 = 50e^{-6000t} + 10e^{-4000t}$$


$$3 = 5e^{-6000t} + e^{-4000t}$$

By trial and error

$$t = 123.1 \mu\text{s}$$

P 5.40 [a]  $i_o(0^-) = 0$  since the switch is open for  $t < 0$ .

[b] For  $t = 0^-$  the circuit is:

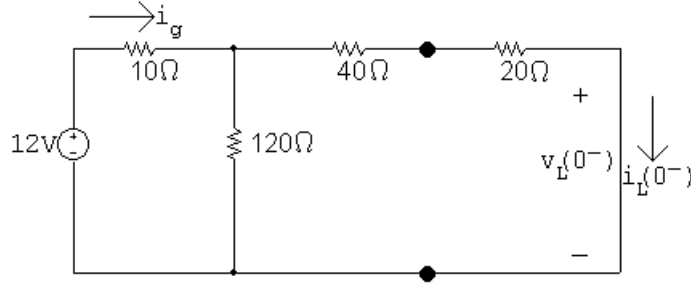


$$120\Omega // 60\Omega = 40\Omega$$

$$\therefore i_g = \frac{12}{10 + 40} = 0.24\text{ A} = 240\text{ mA}$$

$$i_L(0^-) = \left(\frac{120}{180}\right) i_g = 160\text{ mA}$$

[c] For  $t = 0^+$  the circuit is:

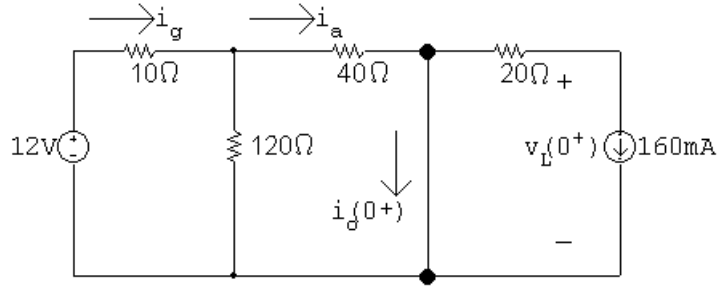

$$120\Omega // 40\Omega = 30\Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30\text{ A} = 300\text{ mA}$$

$$i_a = \left(\frac{120}{160}\right) 300 = 225\text{ mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65\text{ mA}$$

[d]  $i_L(0^+) = i_L(0^-) = 160\text{ mA}$

[e]  $i_o(\infty) = i_a = 225\text{ mA}$

[f]  $i_L(\infty) = 0$ , since the switch short circuits the branch containing the  $20\Omega$  resistor and the  $100\text{ mH}$  inductor.

[g]  $\tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5\text{ ms}; \quad \frac{1}{\tau} = 200$

$$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t}\text{ mA}, \quad t \geq 0$$

[h]  $v_L(0^-) = 0$  since for  $t < 0$  the current in the inductor is constant

[i] Refer to the circuit at  $t = 0^+$  and note:


$$20(0.16) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -3.2 \text{ V}$$

[j]  $v_L(\infty) = 0$ , since the current in the inductor is a constant at  $t = \infty$ .


$$[\mathbf{k}] \quad v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{l}] \quad i_o = i_a - i_L = 225 - 160e^{-200t} \text{ mA}, \quad t \geq 0^+$$


P 5.41 [a]  $t < 0$ :

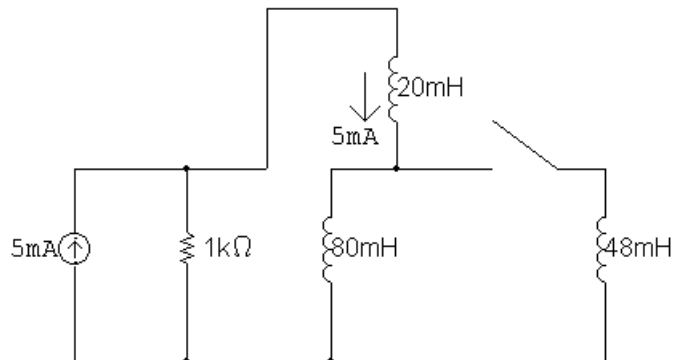

$t = 0^+$ :

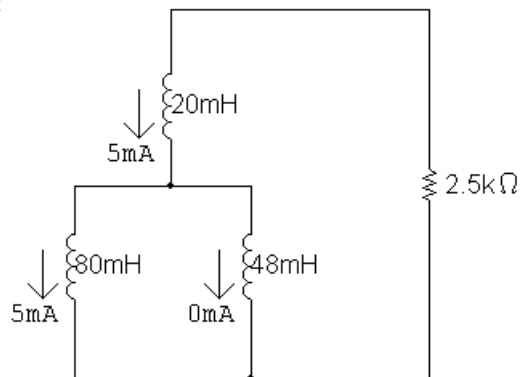


$t > 0$ :

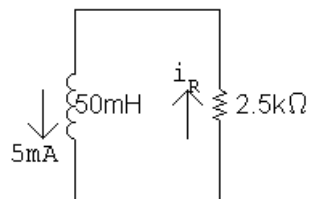

$$i_R = 5e^{t/\tau} \text{ mA}; \quad \tau = \frac{L}{R} = 20 \times 10^{-6}$$

$$i_R = 5e^{-50,000t} \text{ mA}$$

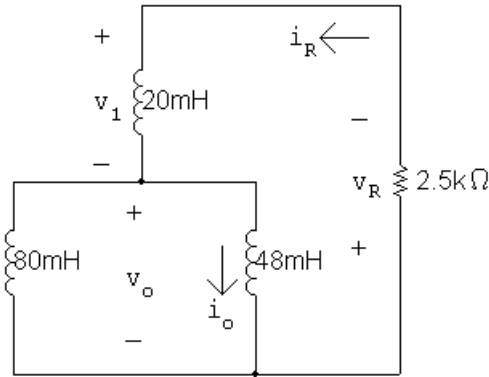

$$v_R = (2.5 \times 10^3)(5 \times 10^{-3})e^{-50,000t} = 12.5e^{-50,000t} \text{ V}$$

$$v_1 = 20 \times 10^{-3}[5 \times 10^{-3}(-50,000)e^{-50,000t}] = -5e^{-50,000t} \text{ V}$$

$$v_o = -v_1 - v_R = -7.5e^{-50,000t} \text{ V}$$

$$\text{[b]} \quad i_o = \frac{10^3}{48} \int_0^t -7.5e^{-50,000x} dx + 0 = 3.125e^{-50,000t} - 3.125 \text{ mA}$$

P 5.42 [a] From the solution to Problem 5.41,

$$i_R = 5 \times 10^{-3}e^{-50,000t} \text{ A}$$

$$p_R = (25 \times 10^{-6}e^{-100,000t})(2.5 \times 10^3) = 62.5 \times 10^{-3}e^{-100,000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^\infty 62.5 \times 10^{-3}e^{-100,000t} dt \\ &= 62.5 \times 10^{-3} \frac{e^{-100,000t}}{-10^5} \bigg|_0^\infty = 625 \text{ nJ} \end{aligned}$$

$$\text{[b]} \quad w_{\text{trapped}} = \frac{1}{2}L_{\text{eq}}i_R^2(0) = \frac{1}{2}(50 \times 10^{-3})(5 \times 10^{-3})^2 = 625 \text{ nJ}$$

CHECK:



$$w(0) = \frac{1}{2}(20)(25 \times 10^{-6}) \times 10^{-3} + \frac{1}{2}(80)(25 \times 10^{-6}) \times 10^{-3} = 1250 \text{ nJ}$$

$$\therefore w(0) = w_{\text{diss}} + w_{\text{trapped}}$$

P 5.43 [a]  $i_L(0) = \frac{80}{40} = 2 \text{ A}$

$$i_o(0^+) = \frac{80}{20} - 2 = 4 - 2 = 2 \text{ A}$$
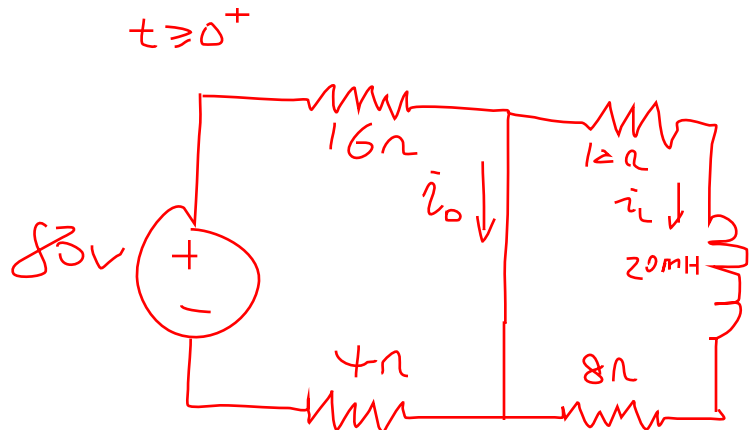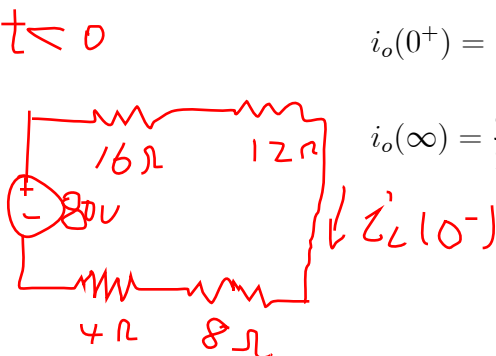
$$i_o(\infty) = \frac{80}{20} = 4 \text{ A}$$



[b]  $i_L = 2e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{20}{20} \times 10^{-3} = 1 \text{ ms}$

$$i_L = 2e^{-1000t} \text{ A}$$


$$i_o = 4 - i_L = 4 - 2e^{-1000t} \text{ A}, \quad t \geq 0^+$$

[c]  $4 - 2e^{-1000t} = 3.8$

$$0.2 = 2e^{-1000t}$$


$$e^{1000t} = 10 \quad \therefore t = 2.30 \text{ ms}$$

P 5.44 [a]  $t < 0$

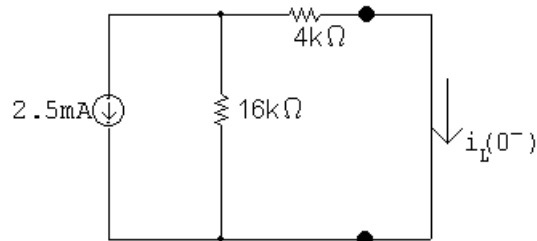

$$i_L(0^-) = \frac{-2.5(16)}{(20)} = -2 \text{ mA}$$

$t \geq 0$

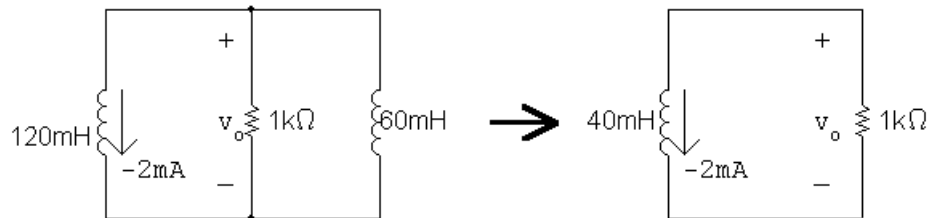

$$\tau = \frac{40 \times 10^{-3}}{10^3} = 40 \times 10^{-6}; \quad 1/\tau = 25,000$$

$$v_o = -1000(-2 \times 10^{-3})e^{-25,000t} = 2e^{-25,000t} \text{ V}, \quad t \geq 0^+$$

[b]  $w_{\text{del}} = \frac{1}{2}(40 \times 10^{-3})(4 \times 10^{-6}) = 80 \text{ nJ}$

[c]  $0.95w_{\text{del}} = 76 \text{ nJ}$


$$\therefore 76 \times 10^{-9} = \int_0^{t_o} \frac{4e^{-50,000t}}{1000} dt$$

$$\therefore 76 \times 10^{-9} = 80 \times 10^{-9} e^{-50,000t} \Big|_0^{t_o} = 80 \times 10^{-9} (1 - e^{-50,000t_o})$$


$$\therefore e^{-50,000t_o} = 0.05$$

$$50,000t_o = \ln 20 \quad \text{so} \quad t_o = 59.9 \mu\text{s}$$

$$\therefore \frac{t_o}{\tau} = \frac{59.9}{40} = 1.498 \quad \text{so} \quad t_o \approx 1.5\tau$$

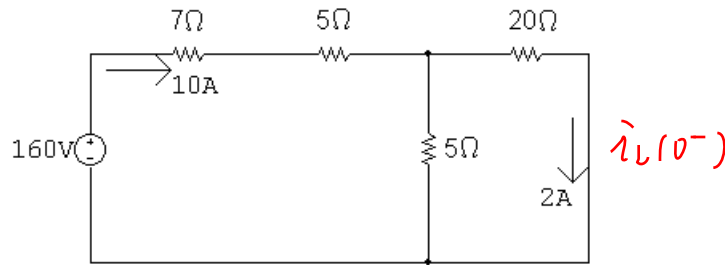P 5.45  $t < 0$ :

$$i_L(0^+) = 2 \text{ A}$$

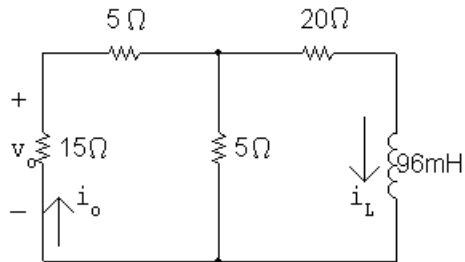 $t > 0$ :

$$R_e = \frac{(20)(5)}{25} + 20 = 24 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{96}{24} \times 10^{-3} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 2e^{-250t} \text{ A}$$

$$\therefore i_o = \frac{5}{25}i_L = 0.4e^{-250t} \text{ A}$$

$$v_o = -15i_o = -6e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$\text{P 5.46} \quad p_{20\Omega} = 20i_L^2 = 20(4)(e^{-250t})^2 = 80e^{-500t} \text{ W}$$

$$w_{20\Omega} = \int_0^\infty 80e^{-500t} dt = 80 \frac{e^{-500t}}{-500} \Big|_0^\infty = 160 \text{ mJ}$$

$$w(0) = \frac{1}{2}(96)(10^{-3})(4) = 192 \text{ mJ}$$

$$\% \text{ diss} = \frac{160}{192}(100) = 83.33\%$$



$$\text{P 5.47} \quad w(0) = \frac{1}{2}(20 \times 10^{-3})(10^2) = 1 \text{ J}$$

$$0.5w(0) = 0.5 \text{ J}$$

$$i_R = 10e^{-t/\tau}$$

$$p_{\text{diss}} = i_R^2 R = 100Re^{-2t/\tau}$$

$$w_{\text{diss}} = \int_0^t R(100)e^{-2x/\tau} dx$$

$$w_{\text{diss}} = 100R \frac{e^{-2x/\tau}}{-2/\tau} \Big|_0^{t_o} = -50\tau R(e^{-2t_o/\tau} - 1) = 50L(1 - e^{-2t_o/\tau})$$

$$50L = (50)(20) \times 10^{-3} = 1; \quad t_o = 10 \mu\text{s}$$

$$1 - e^{-2t_o/\tau} = 0.5$$

$$e^{2t_o/\tau} = 2; \quad \frac{2t_o}{\tau} = \frac{2t_o R}{L} = \ln 2$$

$$R = \frac{L \ln 2}{2t_o} = \frac{20 \times 10^{-3} \ln 2}{20 \times 10^{-6}} = 693.15 \Omega$$

$$\text{P 5.48} \quad [\mathbf{a}] \quad w(0) = \frac{1}{2}LI_g^2$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{t_o} I_g^2 R e^{-2t/\tau} dt = I_g^2 R \frac{e^{-2t/\tau}}{(-2/\tau)} \Big|_0^{t_o} \\ &= \frac{1}{2} I_g^2 R \tau (1 - e^{-2t_o/\tau}) = \frac{1}{2} I_g^2 L (1 - e^{-2t_o/\tau}) \end{aligned}$$

$$w_{\text{diss}} = \sigma w(0)$$

$$\therefore \frac{1}{2} L I_g^2 (1 - e^{-2t_o/\tau}) = \tau \left( \frac{1}{2} L I_g^2 \right)$$

$$1 - e^{-2t_o/\tau} = \sigma; \quad e^{2t_o/\tau} = \frac{1}{(1 - \sigma)}$$

$$\frac{2t_o}{\tau} = \ln \left[ \frac{1}{(1 - \sigma)} \right]; \quad \frac{R(2t_o)}{L} = \ln[1/(1 - \sigma)]$$

$$R = \frac{L \ln[1/(1 - \sigma)]}{2t_o}$$

$$\text{[b]} \quad R = \frac{(20 \times 10^{-3}) \ln[1/0.5]}{20 \times 10^{-6}}$$

$$R = 693.15 \, \Omega$$

P 5.49 [a]  $v_o(t) = v_o(0^+)e^{-t/\tau}$

$$\therefore v_o(0^+)e^{-5 \times 10^{-3}/\tau} = 0.25v_o(0^+)$$

$$\therefore e^{5 \times 10^{-3}/\tau} = 4$$

$$\therefore \tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{\ln 4}$$

$$\therefore L = \frac{250 \times 10^{-3}}{\ln 4} = 180.34 \text{ mH}$$

[b]  $i_L(0^-) = 60 \left( \frac{1}{6} \right) = 10 \text{ mA} = i_L(0^+)$

$$w_{\text{stored}} = \frac{1}{2} L i_L(0^+)^2 = \frac{1}{2} (R\tau) (100 \times 10^{-6}) = 2500\tau \, \mu\text{J}.$$

$$i_L(t) = 10e^{-t/\tau} \text{ mA}$$

$$p_{50\Omega} = i_L^2(50) = 5000 \times 10^{-6} e^{-2t/\tau}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{5 \times 10^{-3}} 5000 \times 10^{-6} e^{-2t/\tau} dt \\ &= 5000 \times 10^{-6} \left. \frac{e^{-2t/\tau}}{(-2/\tau)} \right|_0^{5 \times 10^{-3}} \\ &= 2500 \times 10^{-6} \tau \left[ 1 - e^{\frac{-10 \times 10^{-3}}{\tau}} \right] \end{aligned}$$


$$e^{\frac{-10 \times 10^{-3}}{\tau}} = e^{-2 \ln 4} = 0.0625$$

$$w_{\text{diss}} = 2500 \times 10^{-6} \tau (0.9375)$$

$$\% \text{ diss} = \frac{2500 \times 10^{-6} \tau (0.9375)}{2500 \times 10^{-6} \tau} \times 100$$

$$w_{\text{diss}} = 93.75\%$$


P 5.50 [a]  $t < 0$

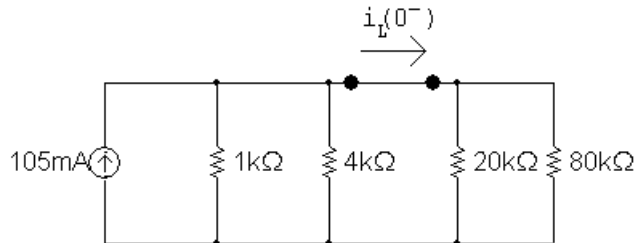

$$1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$$


$$20\text{ k}\Omega \parallel 80\text{ k}\Omega = 16\text{ k}\Omega$$

$$(105)(0.8) = 84\text{ V}$$

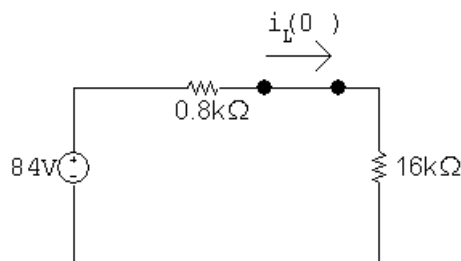

$$i_L(0^-) = \frac{84}{16.8} = 5\text{ mA}$$

$$t > 0$$

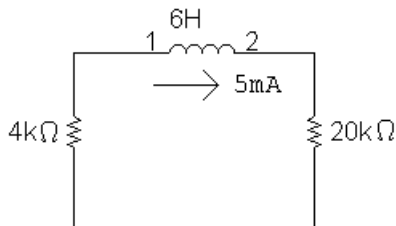

$$\tau = \frac{L}{R} = \frac{6}{24} \times 10^{-3} = 250\text{ }\mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L(t) = 5e^{-4000t}\text{ mA}, \quad t \geq 0$$

$$p_{4k} = 25 \times 10^{-6} e^{-8000t} (4000) = 0.10e^{-8000t}\text{ W}$$

$$w_{\text{diss}} = \int_0^t 0.10e^{-8000x} dx = 12.5 \times 10^{-6} [1 - e^{-8000t}]\text{ J}$$

$$w(0) = \frac{1}{2}(6)(25 \times 10^{-6}) = 75\text{ }\mu\text{J}$$

$$0.10w(0) = 7.5\text{ }\mu\text{J}$$

$$12.5(1 - e^{-8000t}) = 7.5; \quad \therefore e^{8000t} = 2.5$$

$$t = \frac{\ln 2.5}{8000} = 114.54\text{ }\mu\text{s}$$

$$\text{[b]} \quad w_{\text{diss}}(\text{total}) = 75(1 - e^{-8000t})\text{ }\mu\text{J}$$

$$w_{\text{diss}}(114.54\text{ }\mu\text{s}) = 45\text{ }\mu\text{J}$$

$$\% = (45/75)(100) = 60\%$$

$$\text{P 5.51 [a]} \quad R = \frac{v}{i} = 20\text{ k}\Omega$$

$$[\mathbf{b}] \quad \frac{1}{\tau} = \frac{1}{RC} = 1000; \quad C = \frac{1}{(10^3)(20 \times 10^3)} = 0.05 \mu\text{F}$$

$$[\mathbf{c}] \quad \tau = \frac{1}{1000} = 1 \text{ ms}$$

$$[\mathbf{d}] \quad w(0) = \frac{1}{2}(0.05 \times 10^{-6})(10^4) = 250 \mu\text{J}$$

[\mathbf{e}]

$$\begin{aligned} W_{\text{diss}} &= \int_0^{t_o} \frac{v^2}{R} dt = \int_0^{t_o} \frac{(10^4)e^{-2000t}}{(20 \times 10^3)} dt \\ &= 0.5 \frac{e^{-2000t}}{-2000} \Big|_0^{t_o} = 250(1 - e^{-2000t_o}) \mu\text{J} \end{aligned}$$


$$200 = 250(1 - e^{-2000t_o})$$

$$\therefore e^{-2000t_o} = 0.2; \quad e^{2000t_o} = 5$$

$$t_o = \frac{1}{2000} \ln 5; \quad t_o \cong 804.72 \mu\text{s}$$


P 5.52    [\mathbf{a}]     $v_1(0^-) = v_1(0^+) = 75 \text{ V} \quad v_2(0^+) = 0$
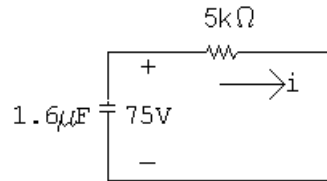
$$C_{\text{eq}} = 2 \times 8/10 = 1.6 \mu\text{F}$$



$$\tau = (5)(1.6) \times 10^{-3} = 8 \text{ ms}; \quad \frac{1}{\tau} = 125$$
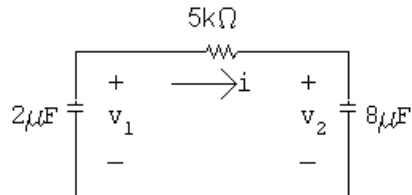
$$i = \frac{75}{5} \times 10^{-3} e^{-125t} = 15e^{-125t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-10^6}{2} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 75 = 60e^{-125t} + 15 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{10^6}{8} \int_0^t 15 \times 10^{-3} e^{-125x} dx + 0 = -15e^{-125t} + 15 \text{ V}, \quad t \geq 0$$


$$[\mathbf{b}] \quad w(0) = \frac{1}{2}(2 \times 10^{-6})(5625) = 5625 \mu\text{J}$$

$$[\mathbf{c}] \quad w_{\text{trapped}} = \frac{1}{2}(2 \times 10^{-6})(225) + \frac{1}{2}(8 \times 10^{-6})225 = 1125 \mu\text{J}.$$

$$w_{\text{diss}} = \frac{1}{2}(1.6 \times 10^{-6})(5625) = 4500 \mu\text{J}.$$

$$\text{Check: } w_{\text{trapped}} + w_{\text{diss}} = 1125 + 4500 = 5625 \mu\text{J}; \quad w(0) = 5625 \mu\text{J}.$$

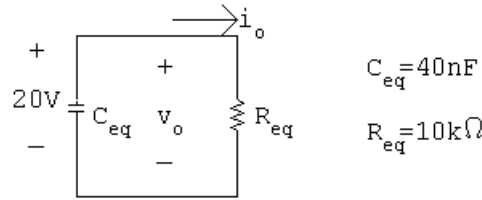P 5.53    **[a]** The equivalent circuit for  $t > 0$ :



$$\tau = 0.4 \text{ ms}; \quad 1/\tau = 2500$$

$$v_o = 20e^{-2500t} \text{ V}, \quad t \geq 0$$

$$i_o = 2e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{25\text{k}\Omega} = 2e^{-2500t} \left( \frac{15}{40} \right) = 0.75e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{25\text{k}\Omega} = (0.5625 \times 10^{-6} e^{-5000t})(25,000) = 14,062.5 \times 10^{-6} e^{-5000t} \text{ W}$$

$$w_{25\text{k}\Omega} = \int_0^\infty 14,062.5 \times 10^{-6} e^{-5000t} dt = -2.8125 \times 10^{-6} (0 - 1) = 2.8125 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.2 \times 10^{-6})(100) + \frac{1}{2}(0.05 \times 10^{-6})(900) = 32.5 \mu\text{J}$$

$$\% \text{ diss } (25 \text{ k}\Omega) = \frac{2.8125}{32.5} \times 100 = 8.65\%$$

$$[\mathbf{b}] \quad p_{625\Omega} = 625(2 \times 10^{-3} e^{-2500t})^2 = 2.5 \times 10^{-3} e^{-5000t}$$

$$w_{625\Omega} = \int_0^\infty p_{625} dt = 0.50 \mu\text{J}$$

$$\% \text{ diss } (625\Omega) = \frac{0.5}{32.5} \times 100 = 1.54\%$$

$$i_{15\text{k}\Omega} = 2e^{-2500t} \left( \frac{25}{40} \right) = 1.25e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{15\text{k}\Omega} = (1.25 \times 10^{-3} e^{-2500t})^2 (15,000) = 23.4375 \times 10^{-3} e^{-5000t} \text{ W}$$

$$w_{15\text{k}\Omega} = \int_0^\infty 23.4375 \times 10^{-3} e^{-5000t} dt = 4.6875 \mu\text{J}$$

$$\% \text{ diss } (15\text{k}\Omega) = 14.42\%$$

$$[\mathbf{c}] \quad \sum w_{\text{diss}} = 2.8125 + 0.50 + 4.6875 = 8 \mu\text{J}$$

$$w_{\text{trapped}} = w(0) - \sum w_{\text{diss}} = 32.5 - 8 = 24.5 \mu\text{J}$$


$$\% \text{ trapped} = \frac{24.5}{32.5} \times 100 = 75.38\%$$

$$\text{Check: } 8.65 + 1.54 + 14.42 + 75.38 = 99.99 \approx 100\%$$

$$\text{P 5.54 } [\mathbf{a}] \quad \frac{1}{C_e} = 1 + \frac{1}{4} = 1.25$$

$$\therefore C_e = 0.8 \mu\text{F}; \quad v_o(0) = 60 - 10 = 50 \text{ V}$$
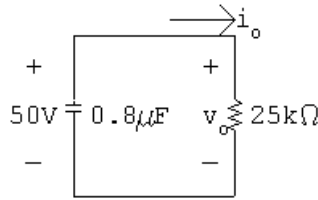
$$\tau = (0.8)(25) \times 10^{-3} = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$



$$v_o = 50e^{-50t} \text{ V}, \quad t > 0^+$$

$$[\mathbf{b}] \quad w_o = \frac{1}{2}(1 \times 10^{-6})(3600) + \frac{1}{2}(4 \times 10^{-6})(100) = 2 \text{ mJ}$$

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(2500) = 1 \text{ mJ}$$

$$\% \text{ diss} = \frac{1}{2} \times 100 = 50\%$$

$$[\mathbf{c}] \quad i_o = \frac{v_o}{25} \times 10^{-3} - 2e^{-50t} \text{ mA}$$

$$\begin{aligned} v_1 &= -\frac{10^6}{4} \int_0^t 2 \times 10^{-3} e^{-50x} dx - 10 = -500 \int_0^t e^{-50x} dx - 10 \\ &= -500 \left. \frac{e^{-50x}}{-50} \right|_0^t - 10 = 10e^{-50t} - 20 \text{ V} \quad t \geq 0 \end{aligned}$$


$$[\mathbf{d}] \quad v_1 + v_2 = v_o$$

$$v_2 = v_o - v_1 = 50e^{-50t} - 10e^{-50t} + 20 = 40e^{-50t} + 20 \text{ V} \quad t \geq 0$$

$$[\mathbf{e}] \quad w_{\text{trapped}} = \frac{1}{2}(4 \times 10^{-6})(400) + \frac{1}{2}(1 \times 10^{-6})(400) = 1 \text{ mJ}$$

$$w_{\text{diss}} + w_{\text{trapped}} = 2 \text{ mJ} \quad (\text{check})$$

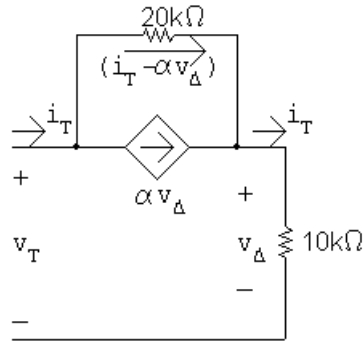P 5.55 [a]  $\tau = RC = R_{Th}(0.2) \times 10^{-6} = 10^{-3}; \quad \therefore R_{Th} = \frac{1000}{0.2} = 5 \text{ k}\Omega$



$$v_T = 20 \times 10^3(i_T - \alpha v_\Delta) + 10 \times 10^3 i_T$$


$$v_\Delta = 10 \times 10^3 i_T$$

$$v_T = 30 \times 10^3 i_T - 20 \times 10^3 \alpha 10 \times 10^3 i_T$$


$$\frac{v_T}{i_T} = 30 \times 10^3 - 200 \times 10^6 \alpha = 5 \times 10^3$$

$$\therefore 30 - 200,000\alpha = 5; \quad \alpha = 125 \times 10^{-6} \text{ A/V}$$

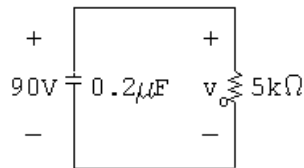[b]  $v_o(0) = (0.018)(5000) = 90 \text{ V} \quad t < 0$   
 $t > 0:$


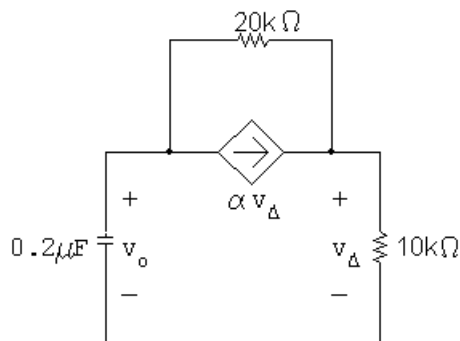
$$v_o = 90e^{-1000t} \text{ V}, \quad t \geq 0$$




$$\frac{v_\Delta}{10 \times 10^3} + \frac{v_\Delta - v_o}{20,000} - 125 \times 10^{-6} v_\Delta = 0$$

$$2v_\Delta + v_\Delta - v_o - 2500 \times 10^{-3} v_\Delta = 0$$

$$\therefore v_\Delta = 2v_o = 180e^{-1000t} \text{ V}$$

P 5.56 [a]

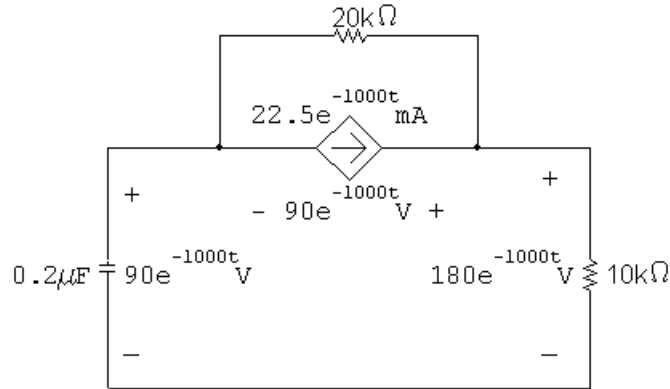

$$p_{ds} = (-90e^{-1000t})(22.5 \times 10^{-3}e^{-1000t}) = -2025 \times 10^{-3}e^{-2000t} \text{ W}$$

$$w_{ds} = \int_0^{\infty} p_{ds} dt = -1012.5 \mu\text{J}.$$

$\therefore$  dependent source is delivering  $1012.5 \mu\text{J}$

$$\text{[b]} \quad p_{10k} = \frac{(180)^2 e^{-2000t}}{10 \times 10^3}$$

$$w_{10k} = \int_0^{\infty} p_{10k} dt = 1620 \mu\text{J}$$


$$p_{20k} = \frac{(90)^2 e^{-2000t}}{20 \times 10^3}$$

$$w_{20k} = \int_0^{\infty} p_{20k} dt = 202.5 \mu\text{J}$$

$$w_c(0) = \frac{1}{2}(0.2) \times 10^{-6}(90)^2 = 810 \mu\text{J}$$

$$\sum w_{\text{dev}} = 810 + 1012.5 = 1822.5 \mu\text{J}$$


$$\sum w_{\text{diss}} = 202.5 + 1620 = 1822.5 \mu\text{J}.$$

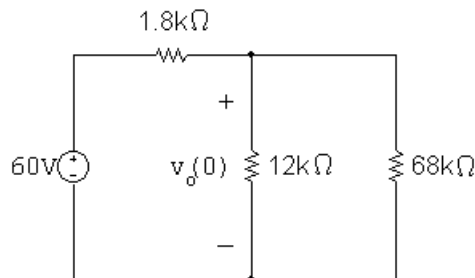P 5.57 [a]  $t < 0$ :

$$v_o(0) = \frac{(60)(10.2)}{12} = 51 \text{ V}$$



$t > 0$ :

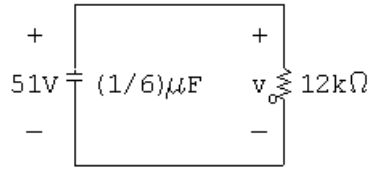

$$\tau = \frac{1}{6}(12) \times 10^{-3} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 51e^{-500t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12} \times 10^{-3} = 216.75 \times 10^{-3} e^{-1000t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{2 \times 10^{-3}} 216.75 \times 10^{-3} e^{-1000t} dt = 216.75 \times 10^{-6} (1 - e^{-2}) \\ &= 187.42 \mu\text{J} \end{aligned}$$

$$[\mathbf{b}] \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{1}{6}\right) (51)^2 \times 10^{-6} = 216.75 \mu\text{J}$$


$$0.95w(0) = 205.9125 \mu\text{J}$$

$$\int_0^{t_o} 216.75 \times 10^{-3} e^{-1000x} dx = 205.9125 \times 10^{-6}$$

$$\int_0^{t_o} e^{-1000x} dx = 0.95 \times 10^{-3}$$

$$\therefore 1 - e^{-1000t_o} = 0.95; \quad e^{1000t_o} = 20; \quad \text{so } t_o = 3 \text{ ms}$$

P 5.58 [a]  $t < 0$ :

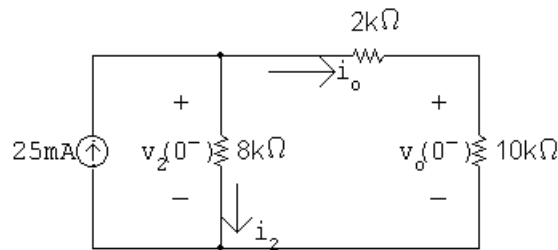


$$i_o(0^-) = \frac{(25)(8)}{(20)} = 10 \text{ mA}$$

$$v_o(0^-) = (10)(10) = 100 \text{ V}$$


$$i_2(0^-) = 25 - 10 = 15 \text{ mA}$$

$$v_2(0^-) = 15(8) = 120 \text{ V}$$

$$t > 0$$

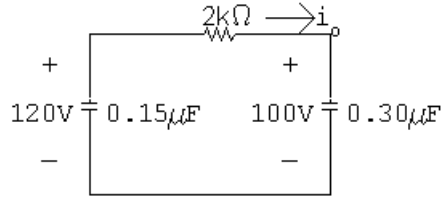

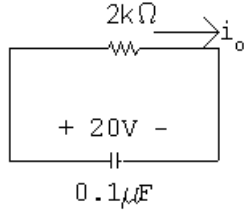
$$\tau = RC = 0.2 \text{ ms} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{20}{2 \times 10^3} e^{-t/\tau} = 10e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

**[b]**

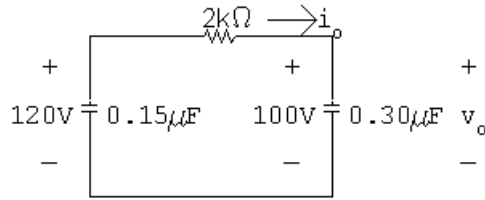

$$\begin{aligned} v_o &= \frac{10^6}{0.3} \int_0^t 10 \times 10^{-3} e^{-5000x} dx + 100 \\ &= \frac{10^5 e^{-5000x}}{3 - 5000} \Big|_0^t + 100 \\ &= -(20/3)e^{-5000t} + (20/3) + 100 \\ v_o &= [-(20/3)e^{-5000t} + (320/3)] \text{ V}, \quad t \geq 0 \end{aligned}$$

**[c]**  $w_{\text{trapped}} = (1/2)(0.15) \times 10^{-6}(320/3)^2 + (1/2)(0.3) \times 10^{-6}(320/3)^2$

$$w_{\text{trapped}} = 2560 \mu\text{J}.$$

Check:

$$w_{\text{diss}} = \frac{1}{2}(0.1 \times 10^{-6})(20)^2 = 20 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.15) \times 10^{-6}(120)^2 + \frac{1}{2}(0.3 \times 10^{-6})(100)^2 = 2580 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$

$$2560 + 20 = 2580 \quad \text{OK.}$$

P 5.59 [a]  $v(0) = \frac{(8)(27)(33)}{60} = 118.80 \text{ V}$

$$R_e = \frac{(3)(6)}{9} = 2 \text{ k}\Omega$$

$$\tau = R_e C = (2000)(0.25) \times 10^{-6} = 500 \mu\text{s}; \quad \frac{1}{\tau} = 2000$$

$$v = 118.80e^{-2000t} \text{ V} \quad t \geq 0$$

$$i_o = \frac{v}{3000} = 39.6e^{-2000t} \text{ mA}, \quad t \geq 0^+$$

[b]  $w(0) = \frac{1}{2}(0.25)(118.80)^2 = 1764.18 \mu\text{J}$

$$i_{4k} = \frac{118.80e^{-2000t}}{6} = 19.8e^{-2000t} \text{ mA}$$


$$p_{4k} = [(19.8)e^{-2000t}]^2(4000) \times 10^{-6} = 1568.16 \times 10^{-3}e^{-4000t}$$

$$w_{4k} = 1568.16 \times 10^{-3} \frac{e^{-4000x}}{-4000} \bigg|_0^{250 \times 10^{-6}} = 392.04(1 - e^{-1}) \mu\text{J}$$

$$= 247.82 \mu\text{J}$$

$$\% = \frac{247.82}{1764.18} \times 100 = 14.05\%$$

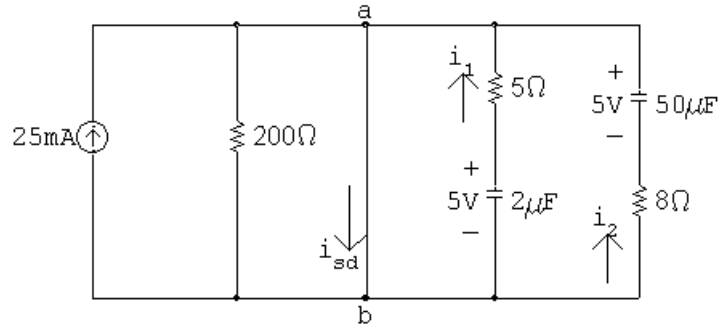P 5.60 [a] At  $t = 0^-$  the voltage on each capacitor will be  $5 \text{ V}(25 \times 10^{-3} \times 200)$ , positive at the upper terminal. Hence at  $t \geq 0^+$  we have



$$\therefore i_{sd}(0^+) = 0.025 + \frac{5}{5} + \frac{5}{8} = 1.65 \text{ A}$$

At  $t = \infty$ , both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 25 \text{ mA}$$

$$[\mathbf{b}] \quad i_{sd}(t) = 0.025 + i_1(t) + i_2(t)$$

$$\tau_1 = (5)(2) \times 10^{-6} = 10 \mu\text{s}$$


$$\tau_2 = (8)(50 \times 10^{-6}) = 400 \mu\text{s}$$

$$\therefore i_1(t) = e^{-10^5 t} \text{ A}, \quad t \geq 0^+$$


$$i_2(t) = 0.625e^{-2500t} \text{ A}, \quad t \geq 0$$

$$\therefore i_{sd} = 25 + 1000e^{-100,000t} + 625e^{-2500t} \text{ mA}, \quad t \geq 0^+$$

P 5.61  $t < 0$

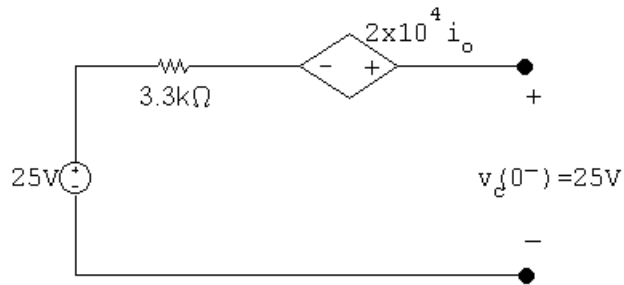


$t > 0$

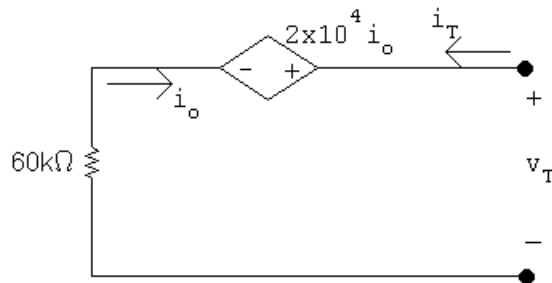

$$\begin{aligned} v_T &= 2 \times 10^4 i_o + 60,000 i_T \\ &= 20,000(-i_T) + 60,000 i_T = 40,000 i_T \end{aligned}$$
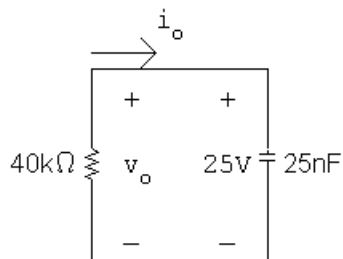
$$\therefore \frac{v_T}{i_T} = R_{\text{Th}} = 40 \text{ k}\Omega$$




$$\tau = RC = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$v_o = 25e^{-1000t} \text{ V}, \quad t \geq 0$$

$$i_o = 25 \times 10^{-9} \frac{d}{dt}[25e^{-1000t}] = -625e^{-1000t} \mu\text{A}, \quad t \geq 0^+$$

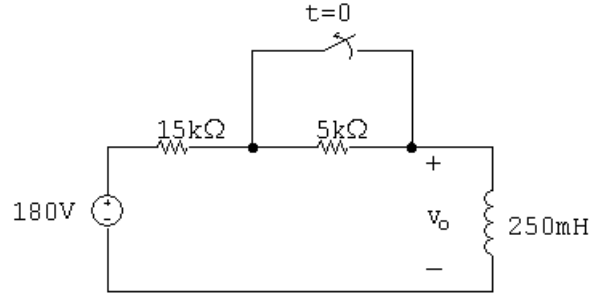P 5.62 After making a Thévenin equivalent we have



$$I_o = 180/15 = 12 \text{ mA}$$

$$\tau = (0.25/20) \times 10^{-3} = 0.125 \times 10^{-4}; \quad \frac{1}{\tau} = 80,000$$

$$\frac{V_s}{R} = \frac{180}{20} = 9 \text{ mA}$$

$$i_o = 9 + (12 - 9)e^{-80,000t} = 9 + 3e^{-80,000t} \text{ mA}$$

$$v = [180 - 12(20)]e^{-80,000t} = -60e^{-80,000t} \text{ V}$$

P 5.63 [a]  $v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-(R_1 + R_2)/L t} \text{ V}, \quad t \geq 0$$

[b]  $v_o = -(12 \times 10^{-3})(5 \times 10^3)e^{-[\frac{15,000+5000}{0.25}]t} = -60e^{-80,000t} \text{ V}, \quad t \geq 0$

[c]  $v_o(0^+) \rightarrow \infty$ , and the duration of  $v_o(t) \rightarrow 0$

[d]  $v_{\text{sw}} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$


Therefore  $i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[ I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-(R_1 + R_2)/L t}$

$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-(R_1 + R_2)/L t}$$

Therefore  $v_{\text{sw}} = \frac{R_1 I_g}{(1 + R_1/R_2)} + \frac{R_2 I_g}{(1 + R_1/R_2)} e^{-(R_1 + R_2)/L t}, \quad t \geq 0$

[e]  $|v_{\text{sw}}(0^+)| \rightarrow \infty$ ; duration  $\rightarrow 0$

P 5.64  $t > 0$

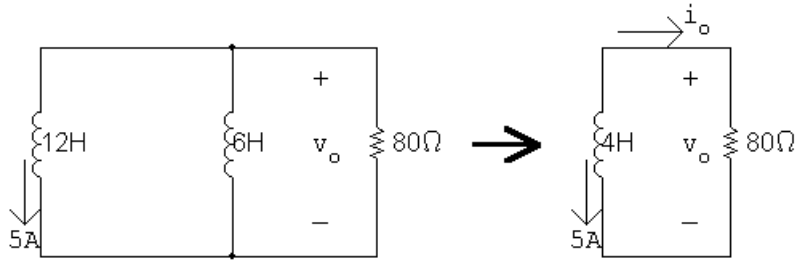

$$\tau = \frac{4}{80} = \frac{1}{20}$$

$$i_o = -5e^{-20t} \text{ A}, \quad t \geq 0$$

$$v_o = 80i_o = -400e^{-20t} \text{ V}, \quad t > 0^+$$

$$-400e^{-20t} = -80; \quad e^{20t} = 5$$

$$\therefore t = \frac{1}{20} \ln 5 = 80.47 \text{ ms}$$

P 5.65 [a]  $w_{\text{diss}} = \frac{1}{2} L_e i^2(0) = \frac{1}{2} (4) (25) = 50 \text{ J}$

[b]


$$\begin{aligned} i_{12H} &= \frac{1}{12} \int_0^t (-400) e^{-20x} dx + 5 \\ &= \frac{-100}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 5 = \frac{5}{3} e^{-20t} + \frac{10}{3} \text{ A} \end{aligned}$$

$$\begin{aligned} i_{6H} &= \frac{1}{6} \int_0^t (-400) e^{-20x} dx + 0 \\ &= \frac{-200}{3} \frac{e^{-20x}}{-20} \Big|_0^t + 0 = \frac{10}{3} e^{-20t} - \frac{10}{3} \text{ A} \end{aligned}$$

$$w_{\text{trapped}} = \frac{1}{2} (18) (100/9) = 100 \text{ J}$$

[c]  $w(0) = \frac{1}{2} (12) (25) = 150 \text{ J}$

P 5.66 [a] For  $t > 0$ :

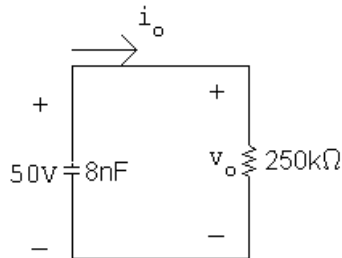

$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 50e^{-500t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad i_o = \frac{v_o}{250} \times 10^{-3} = \frac{50e^{-500t}}{250} \times 10^{-3} = 200e^{-500t} \mu\text{A}$$


$$v_1 = \frac{-10^9}{40} \times 200 \times 10^{-6} \int_0^t e^{-500x} dx + 50 = 10e^{-500t} + 40 \text{ V}, \quad t \geq 0$$

P 5.67     $[\mathbf{a}] \quad w = \frac{1}{2} C_e v_e^2 = \frac{1}{2} (8 \times 10^{-9}) (2500) = 10 \mu\text{J}$

$$[\mathbf{b}] \quad w_{\text{trapped}} = \frac{1}{2} (40)^2 (50) \times 10^{-9} = 40 \mu\text{J}$$

$$[\mathbf{c}] \quad w(0) = \frac{1}{2} (40 \times 10^{-9}) (2500) = 50 \mu\text{J}$$

P 5.68    For  $t < 0$

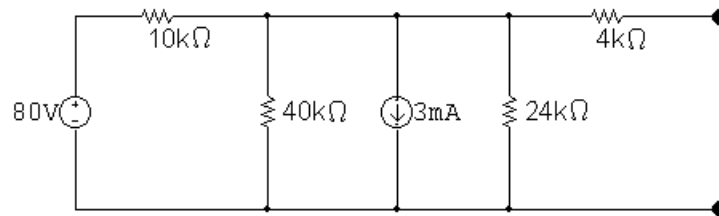


$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$

$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$


$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

$t < 0$

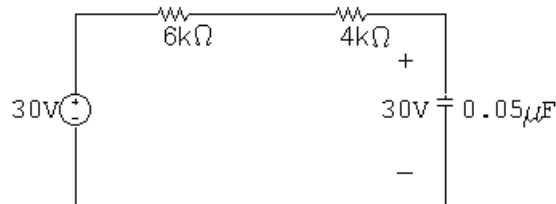


$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

$t > 0$

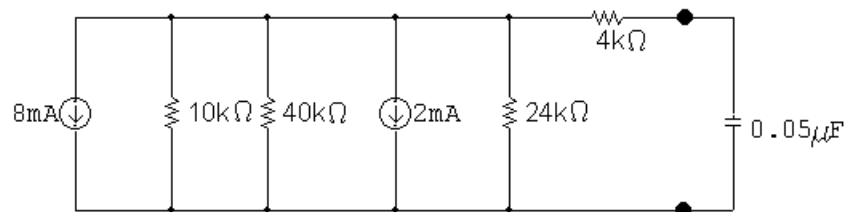
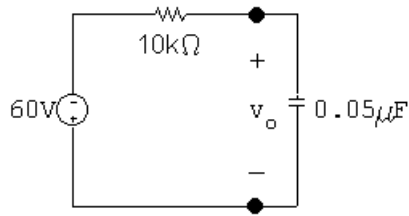
$$v_o(\infty) = -10 \times 10^{-3} (6 \times 10^3) = -60 \text{ V}$$




$$\tau = 0.5 \text{ ms}; \quad \frac{1}{\tau} = 2000$$


$$v_o = -60 + (30 - (-60))e^{-2000t}$$

$$v_o = -60 + 90e^{-2000t} \text{ V} \quad t \geq 0$$

P 5.69 [a]  $t < 0$

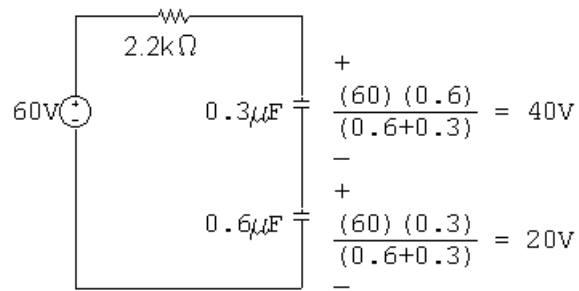

$t > 0$

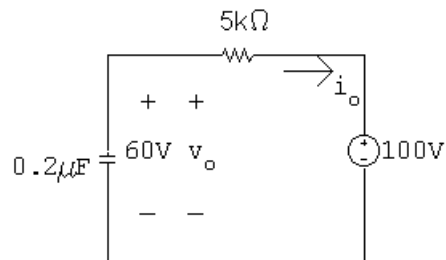

$$v_o(0^-) = v_o(0^+) = 60 \text{ V}$$

$$v_o(\infty) = 100 \text{ V}$$

$$\tau = (0.2)(5) \times 10^{-3} = 1 \text{ ms}; \quad 1/\tau = 1000$$

$$v_o = 100 - 40e^{-1000t} \text{ V}, \quad t \geq 0$$

$$[\text{b}] \quad i_o = -C \frac{dv_o}{dt} = -0.2 \times 10^{-6} [40,000e^{-1000t}]$$

$$= -8e^{-1000t} \text{ mA}; \quad t \geq 0^+$$




$$\begin{aligned}
 \text{[c]} \quad v_1 &= \frac{-10^6}{0.3} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 40 \\
 &= 66.67 - 26.67e^{-1000t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[d]} \quad v_2 &= \frac{-10^6}{0.6} \int_0^t -8 \times 10^{-3} e^{-1000x} dx + 20 \\
 &= 33.33 - 13.33e^{-1000t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\begin{aligned}
 \text{[e]} \quad w_{\text{trapped}} &= \frac{1}{2}(0.3)10^{-6}(66.67)^2 + \frac{1}{2}(0.6)10^{-6}(33.33)^2 \\
 &= 666.67 + 333.33 = 1000 \mu\text{J}.
 \end{aligned}$$

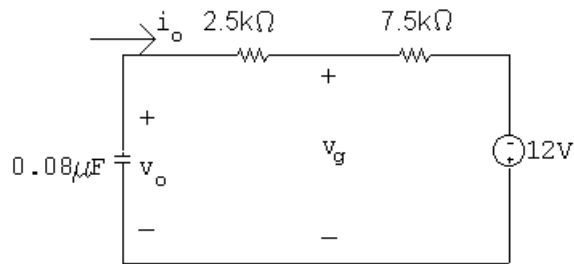P 5.70 [a]  $v_o(0^-) = v_o(0^+) = 48 \text{ V}$



$$v_o(\infty) = -12 \text{ V}; \quad \tau = 0.8 \text{ ms}; \quad \frac{1}{\tau} = 1250$$

$$v_o = -12 + (48 - (-12))e^{-1250t}$$

$$v_o = -12 + 60e^{-1250t} \text{ V}, \quad t \geq 0$$

$$\text{[b]} \quad i_o = -0.08 \times 10^{-6}[-75,000e^{-1250t}]$$

$$i_o = 6e^{-1250t} \text{ mA}, \quad t \geq 0^+$$

$$\text{[c]} \quad v_g = v_o - 2.5 \times 10^3 i_o$$

$$v_g = -12 + 45e^{-1250t} \text{ V}$$

$$\text{[d]} \quad v_g(0^+) = -12 + 45 = 33 \text{ V}$$

Checks:

$$v_g(0^+) = i_o(0^+)7.5 \times 10^3 - 12 = 45 - 12 = 33 \text{ V}$$

$$i_{10k} = \frac{v_g}{10k} = -1.2 + 4.5e^{-1250t} \text{ mA}$$

$$i_{30k} = \frac{v_g}{30k} = -0.4 + 1.5e^{-1250t} \text{ mA}$$

$$-i_o + i_{10} + i_{30} + 1.6 = 0 \quad (\text{ok})$$

P 5.71 [a]  $0 \leq t \leq 1 \text{ ms}$ :

$$v_c(0^+) = 0; \quad v_c(\infty) = 50 \text{ V};$$

$$RC = 400 \times 10^3(0.01 \times 10^{-6}) = 4 \text{ ms}; \quad 1/RC = 250$$

$$v_c = 50 - 50e^{-250t}$$

$$v_o = 50 - 50 + 50e^{-250t} = 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$$1 \text{ ms} \leq t \leq \infty:$$

$$v_c(1 \text{ ms}) = 50 - 50e^{-0.25} = 11.06 \text{ V}$$


$$v_c(\infty) = 0 \text{ V}$$

$$\tau = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_c = 11.06e^{-250(t-0.001)} \text{ V}$$

$$v_o = -v_c = -11.06e^{-250(t-0.001)} \text{ V}, \quad 1 \text{ ms} \leq t \leq \infty$$

[b]

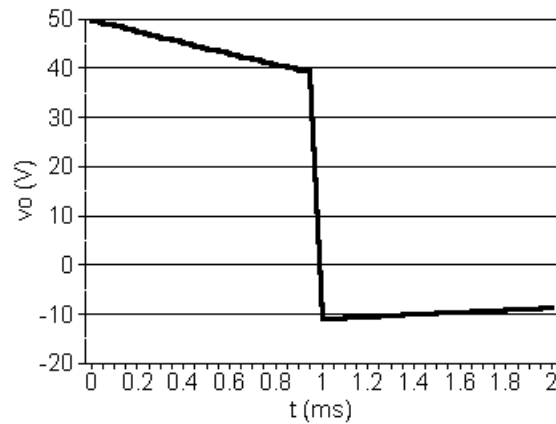P 5.72 [a]  $t < 0$ ;  $v_o = 0$ 

$$0 \leq t \leq 10 \text{ ms}:$$

$$\tau = (50)(0.4) \times 10^{-3} = 20 \text{ ms}; \quad 1/\tau = 50$$

$$v_o = 40 - 40e^{-50t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40(1 - e^{-0.5}) = 15.74 \text{ V}$$

$$10 \text{ ms} \leq t \leq 20 \text{ ms}:$$


$$v_o = -40 + 55.74e^{-50(t-0.01)} \text{ V}$$

$$v_o(20 \text{ ms}) = -40 + 55.74e^{-0.5} = -6.19 \text{ V}$$

$$20 \text{ ms} \leq t \leq \infty:$$

$$v_o = -6.19e^{-50(t-0.02)} \text{ V}$$

[b]

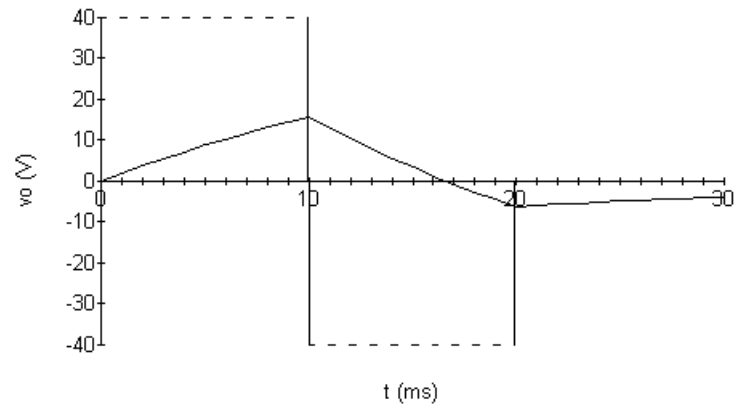[c]  $t \leq 0$  :  $v_o = 0$  $0 \leq t \leq 10$  ms:

$$\tau = 10(0.4 \times 10^{-3}) = 4 \text{ ms}$$

$$v_o = 40 - 40e^{-250t} \text{ V}, \quad 0 \leq t \leq 10 \text{ ms}$$

$$v_o(10 \text{ ms}) = 40 - 40e^{-2.5} = 36.72 \text{ V}$$


 $10 \text{ ms} \leq t \leq 20$  ms:

$$v_o = -40 + 76.72e^{-250(t-0.01)} \text{ V}, \quad 10 \text{ ms} \leq t \leq 20 \text{ ms}$$

$$v_o(20 \text{ ms}) = -40 + 76.72e^{-2.5} = -33.7 \text{ V}$$

 $20 \text{ ms} \leq t \leq \infty$ :
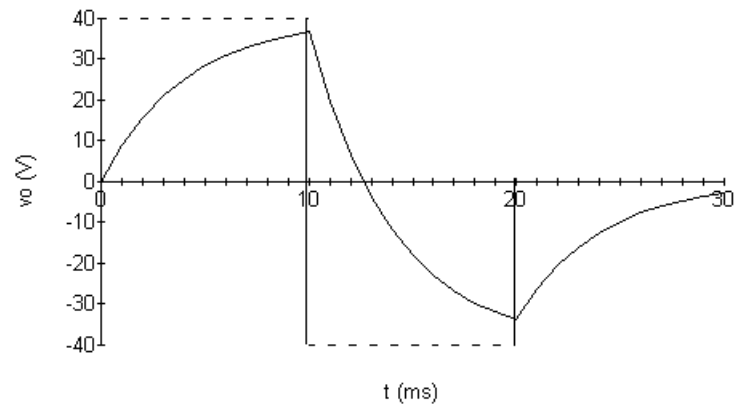
$$v_o = -33.7e^{-250(t-0.02)} \text{ V}, \quad 20 \text{ ms} \leq t \leq \infty$$



P 5.73  $\frac{1}{R_s C_f} = \frac{10^6}{50 \times 10^3(0.05)} = 400$

Therefore,

$$\begin{aligned} v_o &= -400 \int_0^t 75 \cos 5000x \, dx + 0 \\ &= -30,000 \left[ \frac{1}{5000} \sin 5000x \right]_0^t \\ &= -6 \sin 5000t \text{ V} \end{aligned}$$

P 5.74 [a] For  $0 \leq t \leq 25 \text{ ms}$ :

$$\begin{aligned} v_s &= \frac{600}{25}t = 24t \\ \frac{1}{R_s C_f} &= \frac{(10^6)(10^{-3})}{(7.5)(0.16)} = \frac{1000}{1.2} \\ \therefore v_o &= -\frac{1000}{1.2} \int_0^t 24x \, dx + 0 \\ &= -20,000 \left[ \frac{x^2}{2} \right]_0^t \\ &= -10^4 t^2 \text{ V} \quad 0 \leq t \leq 25 \text{ ms} \end{aligned}$$

[b] For  $25 \text{ ms} \leq t \leq 75 \text{ ms}$ :


$$\begin{aligned} v_s &= 1.2 - 24t \\ v_o(25 \text{ ms}) &= -10^4(625 \times 10^{-6}) = -6.25 \text{ V} \\ \therefore v_o &= -\frac{1000}{1.2} \int_{25 \times 10^{-3}}^t (1.2 - 24x) \, dx - 6.25 \\ &= -\frac{1000}{1.2} \left[ 1.2x - \frac{24x^2}{2} \right]_{25 \times 10^{-3}}^t - 6.25 \\ &= 10^4 t^2 - 10^3 t + 12.5 \text{ V} \quad 25 \text{ ms} \leq t \leq 75 \text{ ms} \end{aligned}$$

$$v_o(75 \text{ ms}) = -10^4(5625 \times 10^{-6}) - 75 + 12.5 = -6.25 \text{ V}$$

[c] For  $75 \text{ ms} \leq t \leq 100 \text{ ms}$ :

$$\begin{aligned} v_o &= -\frac{1000}{1.2} \int_{75 \times 10^{-3}}^t (-2.4 + 24x) \, dx - 6.25 \\ &= -10^4 t^2 + 2000t - 100 \text{ V} \quad 75 \text{ ms} \leq t \leq 100 \text{ ms} \end{aligned}$$

[d]

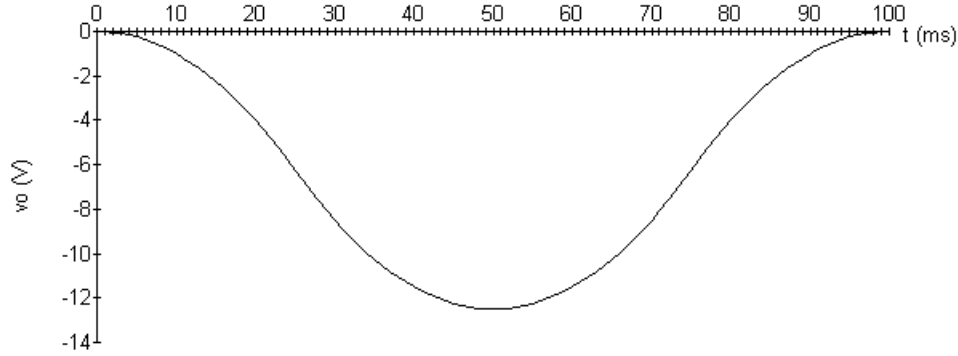

P 5.75 [a]  $v_o(t_1) = \frac{4 \times 10^6}{0.8R}(0.25) = 10$

$$\therefore R = \frac{10^6}{8} = 125 \text{ k}\Omega$$

[b]  $t_2 - t_1 = \frac{4}{10}(250) = 100 \text{ ms}$

P 5.76 [a]  $t_2 - t_1 = \frac{3.6}{10}(250) = 90 \text{ ms}$

$$N_2 = \frac{90}{1000}(10^5) = 9000 \text{ pulses}$$

[b] From (a) we have 9000/3.6 or 2500 pulses/volt.

$$\therefore 7000 \text{ pulses corresponds to } 7000/2500 = 2.8\text{V}$$

$$\therefore v_a = 2.8\text{V}$$

P 5.77 Summing the currents at the inverting input terminal yields

$$\frac{0 - v_{\text{ref}}}{R_{\text{ref}}} + \frac{0 - v_x}{R_x} = 0$$

Solving for  $v_x$  gives

$$v_x = -\left(\frac{V_{\text{ref}}}{R_{\text{ref}}}\right) R_x$$

Since  $(V_{\text{ref}}/R_{\text{ref}})$  is a constant fixed by the circuit designer we see that  $v_x$  is directly proportional to the unknown resistance  $R_x$ .

*This page intentionally left blank*